

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR**  
(AUTONOMOUS)

**B.Tech. III Year I Semester Regular Examinations December-2025**

**DIGITAL CIRCUITS**

(Electrical & Electronics Engineering)

**Time: 3 Hours**

**Max. Marks: 70**

**PART-A**

(Answer all the Questions 10 x 2 = 20 Marks)

- |   |   |  |     |    |    |
|---|---|--|-----|----|----|
| 1 | a | State De-Morgan's theorem.   | CO1 | L1 | 2M |
|   | b | Simplify the following Boolean expression into one literal.<br>$W'X(Z'+YZ) + X(W+Y'Z)$ . | CO2 | L2 | 2M |
|   | c | Determine the Boolean expression for a half adder and full adder.                        | CO2 | L1 | 2M |
|   | d | Convert the binary number 1011 into Gray code.   | CO3 | L1 | 2M |
|   | e | Define a decoder and mention one of its applications.                                    | CO4 | L1 | 2M |
|   | f | State the difference between multiplexer and demultiplexer.                              | CO4 | L1 | 2M |
|   | g | Draw the truth table of an SR latch.   | CO5 | L1 | 2M |
|   | h | Why is the master-slave configuration used in JK flip-flops?                             | CO5 | L1 | 2M |
|   | i | Write the difference between PROM and PLA.   | CO6 | L1 | 2M |
|   | j | Mention two applications of ROM.   | CO6 | L1 | 2M |

**PART-B**

(Answer all Five Units 5 x 10 = 50 Marks)

**UNIT-I**

- |           |   |   |     |    |    |
|-----------|---|---|-----|----|----|
| 2         | a | State and prove the De-Morgan's Theorem with truth tables.  | CO1 | L3 | 5M |
|           | b | State and prove the Consensus theorem.  | CO1 | L3 | 5M |
| <b>OR</b> |   |   |     |    |    |
| 3         | a | Simplify the following expression using the K-map for the 3-variable.<br>$Y = AB'C + A'BC + A'B'C + A'B'C' + AB'C'$ | CO1 | L3 | 5M |
|           | b | Simplify the following Boolean expressions using K-map.<br>$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15)$                | CO1 | L3 | 5M |

**UNIT-II**

- |           |   |   |     |    |     |
|-----------|---|---|-----|----|-----|
| 4         | a | Design & implement Half Adder with truth table.                     | CO3 | L3 | 5M  |
|           | b | Design & implement Full Adder with truth table.                     | CO3 | L3 | 5M  |
| <b>OR</b> |   |   |     |    |     |
| 5         |   | Explain the concept of BCD addition and design a BCD adder circuit. | CO3 | L2 | 10M |

**UNIT-III**

- |           |   |   |     |    |     |
|-----------|---|---|-----|----|-----|
| 6         |   | Minimize the function $F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$ and implement it using an 8-to-1 multiplexer. | CO4 | L2 | 10M |
| <b>OR</b> |   |   |     |    |     |
| 7         | a | Implement the following function $F(A, B, C) = \sum m(1, 3, 5, 6)$ using 16:1 MUX   | CO4 | L2 | 5M  |
|           | b | Implement the following function $F(A, B, C) = \sum m(1, 3, 5, 6)$ using 8:1 MUX  | CO4 | L2 | 5M  |

**UNIT-IV**

- |           |  |  |     |    |     |
|-----------|--|--|-----|----|-----|
| 8         |  | Design a D flip-flop. Explain its truth table and applications.                  | CO5 | L3 | 10M |
| <b>OR</b> |  |  |     |    |     |
| 9         |  | Distinguish between level triggered and edge triggered flip-flops with diagrams. | CO5 | L2 | 10M |

**UNIT-V**

- |           |  |   |     |    |     |
|-----------|--|---|-----|----|-----|
| 10        |  | Compare three combinational circuits: PLA, PAL and PROM.  | CO6 | L3 | 10M |
| <b>OR</b> |  |   |     |    |     |
| 11        |  | Implement PLA circuit for the following functions $F_1(A, B, C) = \sum m(3, 5, 6, 7)$ , $F_2(A, B, C) = \sum m(0, 2, 4, 7)$ . | CO6 | L2 | 10M |

\*\*\* END \*\*\*