

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. III Year I Semester Regular Examinations December-2025

POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | | |
|---|---|--|-----|----|----|
| 1 | a | Define latching current and holding current of a thyristor. | CO1 | L1 | 2M |
| | b | Differentiate between MOSFET and IGBT. | CO1 | L1 | 2M |
| | c | Write the average output voltage equation of a buck converter. | CO3 | L1 | 2M |
| | d | Mention two applications of buck-boost converters. | CO3 | L1 | 2M |
| | e | Define duty ratio in a DC-DC converter. | CO3 | L1 | 2M |
| | f | Write the average output voltage equation of a buck converter. | CO3 | L1 | 2M |
| | g | List the types of PWM techniques used in inverters. | CO4 | L1 | 2M |
| | h | State the principle of operation of a parallel inverter | CO4 | L1 | 2M |
| | i | Derive the RMS load voltage expression for a single-phase AC voltage controller with R load. | CO5 | L2 | 2M |
| | j | Define the integral cycle control. | CO6 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | | |
|---|--|---|-----|----|-----|
| 2 | | Draw and explain the I-V characteristics of a thyristor with neat diagram | CO1 | L2 | 10M |
|---|--|---|-----|----|-----|

OR

- | | | | | | |
|---|--|--|-----|----|-----|
| 3 | | Draw and explain current commutation of a Thyristor. | CO1 | L2 | 10M |
|---|--|--|-----|----|-----|

UNIT-II

- | | | | | | |
|---|--|---|-----|----|-----|
| 4 | | A single Phase fully controlled converter supplies an inductive load. Assuming load current is constant=10A. Determine the following quantities if supply voltage is 230V, 50 Hz and $\alpha=40^\circ$. Calculate the i) Average Output Voltage of converter, ii) Supply RMS Current, iii) Supply Fundamental RMS Current, iv) Fundamental Power factor, v) Supply Power Factor, vi) Supply harmonic factor. | CO2 | L3 | 10M |
|---|--|---|-----|----|-----|

OR

- | | | | | | |
|---|--|--|-----|----|-----|
| 5 | | With circuit and waveforms, explain a Single-Phase Full Bridge Thyristor rectifier with RL loads for Discontinuous Conduction Mode, also derives the average and RMS load voltage. $\alpha=90^\circ$ | CO2 | L2 | 10M |
|---|--|--|-----|----|-----|

UNIT-III

- | | | | | | |
|---|--|---|-----|----|-----|
| 6 | | With average voltage & current, explain the working principle of a boost converter. | CO3 | L2 | 10M |
|---|--|---|-----|----|-----|

OR

- | | | | | | |
|---|--|---|-----|----|-----|
| 7 | | A DC chopper is connected to a 100V DC source supplies an inductive load having 40 mh in series with a resistance of 5ohms. A freewheeling diode is placed across the load. The load current varies between the limits of 10A and 12A. Determine the time ratio of the chopper. | CO3 | L3 | 10M |
|---|--|---|-----|----|-----|

UNIT-IV

- | | | | | | |
|---|--|--|-----|----|-----|
| 8 | | Explain the operation of a single-phase VSI with R-load. | CO4 | L2 | 10M |
|---|--|--|-----|----|-----|

OR

- | | | | | | |
|---|--|--|-----|----|-----|
| 9 | | Illustrate the operation of a three-phase Voltage Source Inverter (VSI) operating in 120° conduction mode. With a neat circuit diagram, voltage and current waveforms, describe the sequence of switching and output phase voltage. | CO4 | L4 | 10M |
|---|--|--|-----|----|-----|

UNIT-V

- | | | | | | |
|----|--|---|-----|----|-----|
| 10 | | The single phase full wave AC voltage controller has a resistive load of $R=5\Omega$ & the input voltage $V_S=120V(RMS)$, 50Hz. The delay angles of thyristors T1 & T2 are equal i.e., $\alpha_1=\alpha_2=2\pi/3$. Determine
(i) The RMS output voltage
(ii) Input power factor
(iii) Average current of thyristor
(iv) The RMS current of thyristor. | CO5 | L3 | 10M |
|----|--|---|-----|----|-----|

OR

- | | | | | | |
|----|--|---|-----|----|-----|
| 11 | | Illustrate the principle of operation of single-phase to single-phase Bridge type step-down cycloconverter with a Resistive Load. | CO5 | L4 | 10M |
|----|--|---|-----|----|-----|

*** END ***

