

SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)

B.Tech. III Year I Semester Regular Examinations December-2025

ANALOG AND DIGITAL IC APPLICATIONS

(Electronics & Communications Engineering)

Time: 3 Hours

Max. Marks: 70

PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- | | | | | |
|-----|---|-----|----|----|
| 1 a | Define an Integrated circuit. | CO1 | L1 | 2M |
| b | State CMRR. | CO1 | L1 | 2M |
| c | Define Virtual Ground property. | CO2 | L1 | 2M |
| d | What is a Schmitt Trigger? | CO3 | L1 | 2M |
| e | Define filter. | CO4 | L1 | 2M |
| f | Write the function of a phase detector. | CO4 | L1 | 2M |
| g | What is voltage regulator? | CO5 | L1 | 2M |
| h | Define ADC. | CO5 | L1 | 2M |
| i | Define PMOS. | CO6 | L1 | 2M |
| j | What is an Encoder? | CO6 | L1 | 2M |

PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

UNIT-I

- | | | | | |
|-----|--|-----|----|----|
| 2 a | Represent the symbol of IC 741 op-amp and Mention the 8 pins.. | CO1 | L1 | 3M |
| b | Draw the Symbol of an Op-Amp and Describe about the Op-Amp. | CO1 | L2 | 7M |

OR

- | | | | | |
|-----|--|-----|----|----|
| 3 a | Illustrate the internal circuit of an operational amplifier | CO1 | L2 | 3M |
| b | Illustrate the block diagram of an operational amplifier and discuss the role of its different stages. | CO1 | L2 | 7M |

UNIT-II

- | | | | | |
|-----|--|-----|----|----|
| 4 a | Illustrate the inverting subtractor using an op-amp, derive the mathematical expression for V_{out} and explain its principle. | CO2 | L3 | 5M |
| b | With the help of an op-amp, derive the working equation for a non-inverting subtractor circuit and discuss its principle. | CO2 | L3 | 5M |

OR

- | | | | | |
|-----|--|-----|----|----|
| 5 a | Describe the principle of a sample and hold circuit with the help of a neat circuit diagram. | CO3 | L2 | 5M |
| b | How logarithmic and antilogarithmic amplifiers are implemented using op-amps? Draw and explain their circuits. | CO3 | L3 | 5M |

UNIT-III

- | | | | | |
|-----|---|-----|----|----|
| 6 a | Explain about the High Pass Filter. | CO4 | L2 | 4M |
| b | Design a 1st Order High Pass Butterworth Filter using an Op-Amp with Expressions. | CO4 | L3 | 6M |

OR

- | | | | | |
|-----|---|-----|----|----|
| 7 a | Design a Low pass filter at a cutoff frequency of 10KHZ with a passband gain of 2. | CO4 | L3 | 5M |
| b | Design a wideband pass filter having $f_L=400\text{HZ}$ $f_H=2\text{KHZ}$ pass band gain of 4. Draw the frequency response of the filter and calculate the Q Value of the filter. | CO4 | L4 | 5M |

UNIT-IV

- | | | | | |
|-----|---|-----|----|----|
| 8 a | Draw and Analyze about the Series Op-Amp Regulator. | CO5 | L4 | 5M |
| b | Explain about the Voltage Regulator. | CO5 | L4 | 5M |

OR

- | | | | | |
|-----|---|-----|----|----|
| 9 a | For a Dual slope ADC $V_R=100\text{mv}$ $t_1=50\text{msec}$ and clock frequency is 12KHZ find the digital output for an input voltage of 200mv. | CO5 | L5 | 5M |
| b | An 8-bit has resolution of 20mv/LSB. find its VOFS and VO if the input is $(10000000)_2$. | CO5 | L5 | 5M |

UNIT-V

- | | | | | |
|-----------|---|-----|----|----|
| 10 a | Draw and Explain about the NMOS Transistors. | CO6 | L3 | 5M |
| b | Draw and Explain about the Basic CMOS Inverter. | CO6 | L3 | 5M |
| OR | | | | |
| 11 a | Draw and Explain about the Priority Encoder. | CO6 | L2 | 5M |
| b | Define Multiplexer and Explain any one of the Multiplexer with truth table. | CO6 | L1 | 5M |

*** END ***

