

## SIDDHARTH INSTITUTE OF ENGINEERING &amp; TECHNOLOGY:: PUTTUR

(AUTONOMOUS)

B.Tech. II Year I Semester Regular &amp; Supplementary Examinations November-2025

## DIGITAL CIRCUITS DESIGN

(Electronics &amp; Communications Engineering)

Time: 3 Hours

Max. Marks: 70

## PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- 1 a List out the types of number systems with one example for each. CO1 L2 2M
- b What are Universal Gates? Give their truth tables. CO1 L1 2M
- c Define Multiplexer and Demultiplexer. CO4 L1 2M
- d Define the following: i) Half adder and ii) Full Adder CO4 L1 2M
- e Differentiate between Verilog and VHDL. CO6 L4 2M
- f What is the Sensitivity list? CO6 L1 2M
- g Difference between Latch and Flip-flop? CO4 L4 2M
- h Write a short note on Register. CO4 L1 2M
- i State the types of ROM. CO2 L1 2M
- j List basic types of programmable logic devices. CO5 L1 2M

## PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

## UNIT-I

- 2 a Convert the following numbers: CO1 L5 5M
- i)  $(AB)_{16} = ( )_2$  ii)  $(1234)_8 = ( )_{16}$  (iii)  $(1000011)_2 = ( )_{10}$
- b Perform the following subtraction by using 1's complement. CO1 L4 5M
- i) 111001-1010 ii) 0011-10001

OR

- 3 Illustrate the digital logic gates with graphical symbol, algebraic function and truth table. CO1 L2 10M

## UNIT-II

- 4 a Simplify the expression in SOP form using don't cares. CO4 L3 5M
- $Y = \Sigma (4,5,6,8,9) + d \Sigma (3,7,10,11,14,15)$
- b Design a 4 bit Binary-to-BCD code converter. CO4 L3 5M

OR

- 5 a Draw the circuit for 3 to 8 decoder and explain. CO4 L2 5M
- b Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table. CO4 L2 5M

## UNIT-III

- 6 a What is the syntax used to write a Verilog Code CO6 L1 4M
- b Write Verilog code to implement the function CO6 L1 6M
- $f(x_1, x_2, x_3) = m(0, 1, 3, 4, 5, 6)$  using the continuous assignment.

OR

- 7 a Write an Verilog code for Full Adder with the help of Truth table. CO6 L1 6M
- b State the importance of CAD Tools in HDL. CO6 L1 4M

## UNIT-IV

- 8 a Compare the differences between combinational and sequential circuits. CO4 L3 5M
- b Differentiate between synchronous and asynchronous sequential circuits. CO4 L2 5M

OR

- 9 Define a Shift register and explain its types. CO4 L2 10M

## UNIT-V

- 10 Derive the simplified sequential circuit for the following state table. CO2 L3 10M

PS	Next State		Output	
	X=0	X=1	X=0	X=1
A	a	b	0	0
B	c	d	0	0
C	a	d	0	0
D	c	f	0	1
E	a	f	0	1
F	g	f	0	1
G	a	f	0	1

OR

- 11 a Draw and Briefly explain the basic structures of CPLD & FPGA. CO5 L2 5M
- b Compare PROM, PLA & PLA. CO5 L4 5M

\*\*\* END \*\*\*