

Time: 3 Hours

Max. Marks: 70

## PART-A

(Answer all the Questions 10 x 2 = 20 Marks)

- 1 a What is balanced voltage and balanced impedance? CO1 L1 2M
- b A star-connected load has  $6 + j8 \Omega$  impedance per phase. Determine the line current if it is connected to 400 V, 3 $\phi$ , 50 Hz supply. CO1 L3 2M
- c Find the Laplace transform of exponential function  $f(t) = e^{at}$ . CO2 L4 2M
- d What is the time constant of an RL circuit? CO2 L1 2M
- e Define z-parameters. CO4 L1 2M
- f What are the short-circuit impedance parameters of a two-port network? CO4 L1 2M
- g What are the conditions which a periodic function must satisfy to have its Fourier series expansion? CO5 L1 2M
- h Write the steps for application of Fourier transform to circuit analysis. CO5 L1 2M
- i Draw constant-k low pass filter and high pass filter. CO6 L3 2M
- j What is a filter? Classify them. CO6 L2 2M

## PART-B

(Answer all Five Units 5 x 10 = 50 Marks)

## UNIT-I

- 2 Discuss in detail the three phase 4-wire circuits with star connected balanced loads and power consumed by a balanced star-connected load. CO1 L2 10M

## OR


- 3 Show that three-phase power can be measured by two wattmeters. Draw the phasor diagrams. Derive an expression for power factor in terms of wattmeter readings. CO1 L1 10M

## UNIT-II

- 4 Derive an expression for the step response in an R-C series circuit excited by DC Supply and write the initial and final condition with characteristics. CO2 L3 10M

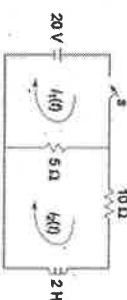
## OR

- 5 For the circuit shown in Figure, determine the current in the  $10\Omega$  resistor when the switch is closed at  $t = 0$ . Assume initial current through the inductor is zero. CO3 L2 10M


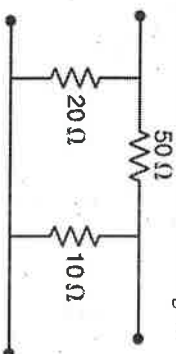
## UNIT-III


- 6 a Find the y-parameters for the network shown in Figure. CO4 L4 4M



- b Develop an equation for Hybrid Parameters ( $h$ -Parameters) and Inverse Hybrid Parameters ( $g$ -Parameters). CO3 L2 6M
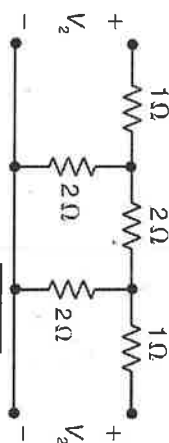
## OR

- 7 a Two two-port networks are connected in cascade. Prove that the overall transmission parameter matrix is the product of individual transmission parameter matrices. CO4 L4 5M
- b Find the transmission parameters for the network shown in Figure considering two networks connected in cascade. CO4 L3 5M




## UNIT-IV

- 8 Stimulate the complex Fourier series for periodic waveform. CO5 L4 10M
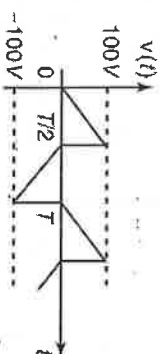
## OR

- 9 Determine the Fourier series of repetitive waveform of Figure shown up to 5<sup>th</sup> harmonic, when time of repetition,  $T = 20$  ms. Calculate the fundamental frequency current, where  $R = 10$  ohms and  $L = 0.0318H$  with voltage transform of the waveform. CO5 L2 10M




## UNIT-V

- 10 a Design the low pass RL filter and illustrate the frequency-phase response curve. CO6 L1 5M
- b Define Band Elimination Filter. Derive the operational characteristics of a band elimination filter. CO6 L1 5M
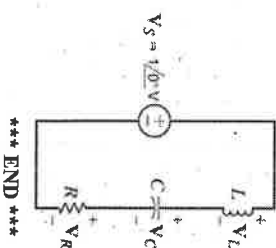
## OR

- 11 Consider the frequency-dependent network in Figure. Given the following circuit parameter values:  $L = 159 \mu H$ ,  $C = 159 \mu F$ , and  $R = 10\Omega$ , let us demonstrate that this one network can be used to produce a low-pass, highpass, or band-pass filter. CO6 L3 10M



\*\*\* END \*\*\*