


SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR
(AUTONOMOUS)

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)
Subject with Code: Electronic Devices and Circuits(23EC0402)

Course & Branch: B.Tech.–ECE

Regulation: R23

Year & Sem: II-B.Tech.& I-Sem.

UNIT –I
PN JUNCTION DIODE AND SPECIAL DIODES

1.	a)	Define efficiency of a rectifier.	[L1] [CO2]	[2M]
	b)	Draw the symbol of SCR, UJT and photo diode.	[L1] [CO2]	[2M]
	c)	Define clipper and list types.	[L1] [CO2]	[2M]
	d)	List the applications of clampers.	[L1] [CO2]	[2M]
	e)	Formulate the Diode current equation.	[L2] [CO2]	[2M]
2.	a)	Explain the construction of PN Junction Diode.	[L2] [CO1]	[4M]
	b)	Illustrate the working of a PN Junction diode under biasing with neat diagrams and draw the VI characteristics.	[L2] [CO1]	[6M]
3.	a)	Discuss the effect of temperature on V-I characteristics of a PN Junction Diode.	[L2] [CO2]	[5M]
	b)	When a reverse bias is applied to a germanium PN Junction Diode, the reverse saturation current at room temperature is $0.3\mu\text{A}$. Determine the current flowing in the diode when 0.3V forward bias is applied at room temperature.	[L3] [CO3]	[5M]
4.	a)	Calculate the forward resistance of a PN Junction Diode when the forward current is 5mA at $T = 300\text{K}$. Assume Silicon diode.	[L3] [CO3]	[5M]
	b)	Discuss the following terms with respect to PN diode i) Transition capacitance ii) Diffusion capacitance iii) forward and reverse resistances	[L2] [CO2]	[5M]
5.	a)	Draw the circuit diagram of a half Wave Rectifier and explain its operation with the help of waveforms.	[L2] [CO4]	[4M]
	b)	Derive the expressions for Average DC Voltage, RMS Value of voltage, DC output Power and AC input Power, Efficiency and Ripple factor for a Half Wave Rectifier.	[L4] [CO4]	[6M]
6.	a)	A Half Wave Rectifier is supplied from a 230V , 50Hz supply with a step-down ratio of $3:1$ to a resistive load of $10\text{k}\Omega$. The diode forward resistance is 75Ω while transformer secondary is 10Ω . Calculate maximum, average, RMS values of current, DC output voltage, efficiency of rectification.	[L4] [CO4]	[5M]
	b)	With the help of neat sketch describe the working of capacitive and inductive filter with full wave rectifier.	[L2] [CO4]	[5M]
7.	a)	Compare Half Wave, Full Wave and Bridge Wave rectifiers.	[L4] [CO4]	[5M]
	b)	A Full Wave Rectifier circuit is fed from a transformer having a centre-tapped secondary winding. The RMS voltage from either end of secondary to centre tap is 30V . If the diode forward	[L4] [CO4]	[5M]


		resistance is 2Ω and that of the half secondary is 8Ω , for a load of $1\text{ K}\Omega$. Calculate DC power delivered to the load, efficiency of rectification.		
8.	a)	Design the Positive and Negative Diode Clippers and explain with neat waveforms.	[L2] [CO5]	[5M]
	b)	What is a Clamper? Describe positive and negative clippers with neat circuit diagram.	[L2] [CO4]	[5M]
9.	a)	Discuss the characteristics of Photo diode with its symbol.	[L2] [CO2]	[3M]
	b)	With neat diagram explain working of SCR and draw the VI characteristics.	[L1] [CO2]	[7M]
10.	a)	Discuss the working of LCD with LED with neat diagrams.	[L2] [CO1]	[5M]
	b)	With basic structure, symbol and equivalent circuit explain working of UJT and draw characteristics.	[L2] [CO2]	[5M]
11.	a)	Explain the working principle of Varactor diode and list its applications.	[L1] [CO1]	[3M]
	b)	Draw the circuit symbol of Tunnel diode. Explain the Volt-Ampere (V-I) characteristics with neat sketch.	[L2] [CO2]	[7M]

UNIT –II


BIPOLAR JUNCTION TRANSISTOR CHARACTERISTICS AND BIASING

1.	a)	What is BJT and Draw its symbol.	[L2] [CO1]	[2M]
	b)	Classify BJT based on construction and define operating regions in BJT.	[L1] [CO2]	[2M]
	c)	List applications of BJT.	[L1] [CO2]	[2M]
	d)	State the need of biasing.	[L2] [CO2]	[2M]
	e)	Mention any three BJT specifications.	[L1] [CO1]	[2M]
2.	a)	With the help neat diagram discuss the operation of NPN and PNP transistor.	[L2] [CO1]	[5M]
	b)	Illustrate the operation of a transistor as an amplifier and as a switch with suitable diagrams.	[L4] [CO3]	[5M]
3.	a)	Derive the relation among α , β and γ of a Transistor.	[L3] [CO5]	[6M]
	b)	If the base current in a transistor is $20\mu\text{A}$, when the emitter current is 6.4mA , what are the values of α and β ? Also calculate the collector current.	[L4] [CO4]	[4M]
4.	a)	With neat circuit diagram, explain the Input and Output characteristics of a BJT in CB Configuration.	[L3] [CO4]	[5M]
	b)	Compare the characteristics of Common Emitter (CE), Common Base (CB), and Common Collector (CC) configurations.	[L2] [CO4]	[5M]
5.	a)	With neat circuit diagram, explain the Input and Output characteristics of a BJT in CC Configuration.	[L2] [CO4]	[5M]
	b)	For a transistor, the leakage current is $0.1\mu\text{A}$ in CB configuration, while it is $19\mu\text{A}$ in CE configuration. Calculate α & β of the same transistor.	[L4] [CO3]	[5M]
6.	a)	Discuss the Input and Output characteristics of a BJT in CE Configuration. Indicate the regions of operations in the output characteristics.	[L3] [CO2]	[6M]
	b)	Explain the limits of operation of BJT.	[L3] [CO1]	[4M]
7.	a)	Describe the DC and AC load lines of a transistor and explain the criteria for determining the Q-point.	[L2] [CO2]	[5M]
	b)	List the different types of transistor biasing methods and explain the Fixed Bias configuration with a neat circuit diagram.	[L2] [CO2]	[5M]
8.	a)	Explain the Collector-to-Base biasing method of a transistor with a neat circuit diagram and derive stability factor.	[L2] [CO4]	[6M]
	b)	Differentiate between NPN and PNP transistors based on their characteristics.	[L3][CO6]	[4M]
9.	a)	Describe the self-bias method of transistor biasing with the help of a neat circuit diagram.	[L2] [CO2]	[5M]
	b)	Derive the stability factors S and S' of a BJT self-bias.	[L2] [CO5]	[5M]
10.	a)	Compare the various biasing techniques of a BJT.	[L3] [CO6]	[4M]
	b)	Consider the self-bias circuit where $V_{CC} = 22.5\text{volts}$, $R_C = 5.6\text{k}\Omega$, $R_2 = 10\text{k}\Omega$ and $R_1 = 90\text{k}\Omega$, $h_{fe} = 55$, $V_{BE} = 0.6\text{V}$. the transistor operates in active region. Determine i) Operating point ii) stability factor.	[L3] [CO2]	[6M]
11.	a)	Discuss Thermal Runaway and derive the expression for thermal Resistance.	[L4] [CO6]	[6M]
	b)	Explain the concept of thermal stability in transistor biasing and discuss the conditions necessary for achieving it.	[L4] [CO2]	[4M]

UNIT –III
BJT SMALL SIGNAL OPERATION AND MODELS

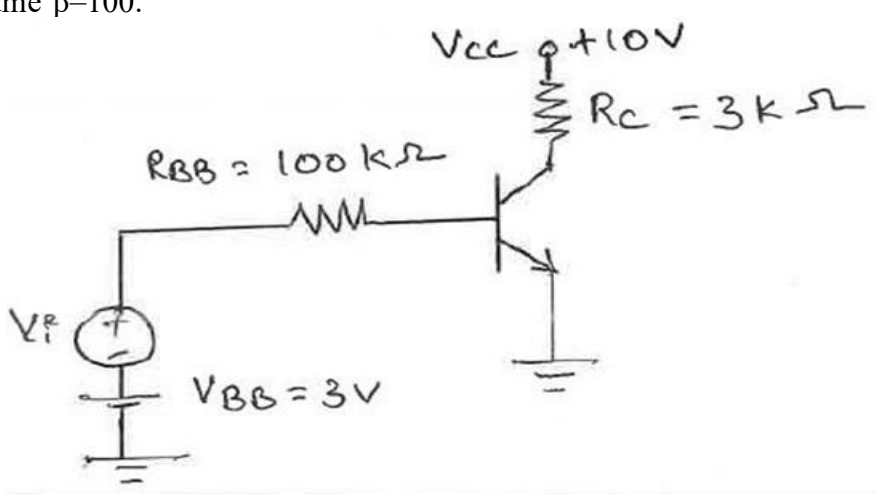
1	a)	Define trans conductance g_m in BJT.	[L1] [CO1]	2M
	b)	Give the expression for r_π (input resistance) in hybrid- π model?	[L2] [CO1]	2M
	c)	Mention the characteristics of CE amplifier.	[L1] [CO1]	2M
	d)	Express the open circuit over all voltage gain of BJT amplifier.	[L2] [CO1]	2M
	e)	List the applications of CC amplifier.	[L1] [CO1]	2M
2	a)	Discuss the need of small-signal analysis in BJT circuits.	[L2] [CO1]	[4M]
	b)	Explain the term thermal voltage V_T and its effect on small-signal model in detail.	[L2] [CO1]	[6M]
3	a)	Derive the transconductance g_m for a given collector current I_C .	[L3] [CO2]	[5M]
	b)	Determine base current and input resistance at Base of BJT.	[L3] [CO1]	[5M]
4	a)	Determine Emitter current and input resistance at Emitter of BJT.	[L3] [CO2]	[5M]
	b)	Describe the process of finding the DC operating point (quiescent point) of a BJT.	[L2] [CO1]	[5M]
5		Evaluate the voltage gain for transistor amplifier as shown in figure below assume $\beta=100$. 	[L5] [CO2]	[10M]
6	a)	With a neat diagram describe the key components of the hybrid- π model of BJT.	[L2] [CO3]	[5M]
	b)	Sketch the T-model of transistor and list out the applications of Small-signal Equivalent circuits.	[L1] [CO3]	[5M]
7	a)	Specify the significance of the base-emitter resistance in the T-model and state its effect on voltage gain.	[L3] [CO2]	[5M]
	b)	Compare the T-model and the hybrid- π model.	[L4] [CO3]	[5M]
8	a)	Discuss the process of separating the signal and the DC quantities with suitable diagrams.	[L2] [CO4]	[6M]
	b)	Define voltage gain and derive A_v for CE amplifier with emitter resistance.	[L1] [CO3]	[4M]
9	a)	Evaluate the small-signal voltage gain A_v , R_i and R_o of a common-emitter amplifier Without an emitter resistor R_E with equivalent circuit.	[L4] [CO4]	[7M]
	b)	List out the characteristics of CE amplifier with emitter resistance.	[L1] [CO1]	[3M]
10	a)	Derive the small-signal voltage gain A_v , R_i and R_o of a common-Base amplifier with Equivalent circuit.	[L2] [CO4]	[5M]
	b)	Design the small-signal, common-collector amplifier with equivalent circuit and explain its working in detail.	[L2] [CO2]	[5M]
11		For the CE amplifier shown in figure $V_{CC} = 9V$, $R_1 = 27 k\Omega$, $R_2 = 15 k\Omega$, $R_E = 1.2 k\Omega$ and $R_C = 2.2 k\Omega$. The transistor has $\beta = 100$, $V_A = 100 V$.	[L3] [CO4]	[10M]

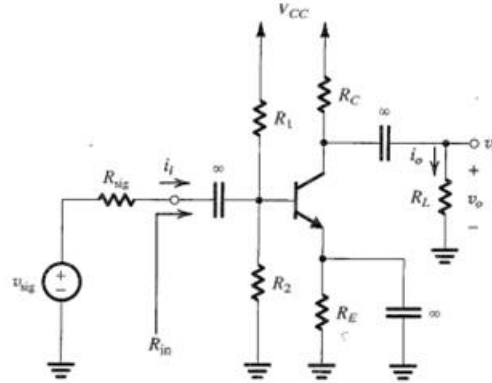Calculate the DC bias current I_E . If the amplifier operates between source for which $R_{sig} = 10\text{ k}\Omega$ and a load of $2\text{ k}\Omega$, replace the transistor with its hybrid π -model, and compute the values of R_{in} , Voltage gain V_o/V_{sig} , and the current gain i_o/i_i .




UNIT- IV

Junction Field Effect Transistor and MOS Field Effect Transistors

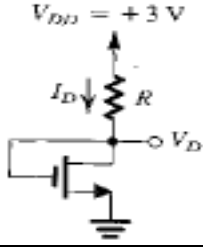1.	a)	Mention the applications of JFET.	[L1] [CO2]	[2M]
	b)	Define Pinch off Voltage.	[L1] [CO2]	[2M]
	c)	Classify the types of JFET with its symbols.	[L1] [CO2]	[2M]
	d)	What is the principle of a MOSFET?	[L1] [CO2]	[2M]
	e)	Draw the CMOS structure.	[L1] [CO2]	[2M]
2.	a)	State the working principle of FET and list important features.	[L1] [CO2]	[4M]
	b)	Explain the construction and working of N-channel JFET.	[L2] [CO2]	[6M]
3.		Elaborate the Transfer and drain characteristics of N-channel JFET with neat sketches.	[L2] [CO4]	[10M]
4.	a)	Explain the process of fixing the Q point in FET?	[L2] [CO2]	[4M]
	b)	Distinguish the features of BJTs and FETs.	[L5] [CO2]	[6M]
5.	a)	Explain JFET works as a voltage variable resistor.	[L4] [CO3]	[6M]
	b)	Classify the types of MOSFET and draw their symbols.	[L2] [CO3]	[4M]
6.	a)	Explain the construction & operation of an enhancement type NMOS Transistor.	[L2] [CO2]	[6M]
	b)	Plot the V-I Characteristics of an n-channel enhancement MOSFET and explain in detail.	[L2] [CO2]	[4M]
7.	a)	Design the circuit in Fig. below to obtain a current I_D of 80 μ A. Find the value required for R, and find the dc voltage V_D . Let the NMOS transistor have $V_t = 0.6$ V, $\mu_n C_{ox} = 200$ μ A/V ² . $L = 0.8$ μ m, and $W = 4$ μ m. Neglect the channel-length modulation effect (i.e., assume $\lambda = 0$). 	[L4] [CO2]	[6M]
	b)	Design a switch using a MOSFET.	[L4] [CO5]	[5M]
8.	a)	Design an amplifier using a MOSFET.	[L4] [CO5]	[6M]
	b)	Consider a process technology for which $L_{min} = 0.4$ μ m, $t_{ox} = 8$ nm, $\mu_n = 450$ cm ² /V-s, and $V_t = 0.7$ V. (i) Calculate C_{ox} and k_n . (ii) For a MOSFET with $W/L = 8$ μ m/ 0.8 μ m, calculate the values of V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 100$ μ A. (iii) For the device in (ii), calculate the value of V_{GS} required to cause the device to operate as a 1000- Ω resistor for very small V_{DS}	[L3] [CO3]	[4M]
9.	a)	Explain the biasing technique by fixing V_{GS} without source resistance for MOSFET amplifier with neat circuit diagram.	[L2] [CO2]	[5M]
	b)	Discuss the biasing technique for MOSFET amplifier using drain to gate feedback resistor in detail.	[L2] [CO4]	[5M]
10.	a)	Explain the concept of modelling of Body Effect.	[L2] [CO2]	[4M]
	b)	Distinguish between Depletion MOSFET and Enhancement MOSFET.	[L5] [CO2]	[6M]
11		Discuss the characteristic parameters of the JFET and show the relation among the JFET parameters μ , r_d and g_m .	[L2] [CO3]	[10M]


UNIT- V

MOSFET SMALL SIGNAL OPERATION MODELS

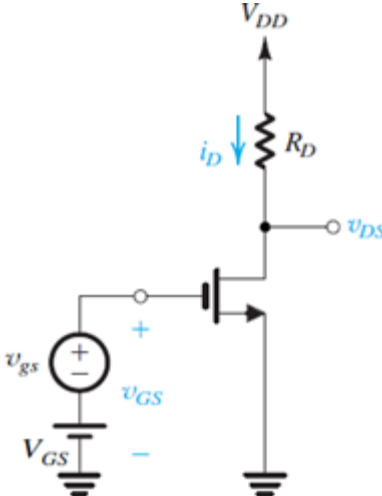
1	a)	List the small-Signal Parameters of MOSFET.	[L1] [CO1]	2M
	b)	Explain the concept of small-signal analysis for a MOSFET.	[L1] [CO4]	2M
	c)	Define Transconductance.	[L1] [CO5]	2M
	d)	Draw an alternative representation of the T model.	[L1] [CO5]	2M
	e)	List the applications of the Small-Signal Equivalent Circuits.	[L1] [CO2]	2M
2	a)	Demonstrate the Small-Signal Operation of the MOSFET amplifier with neat diagrams.	[L2] [CO5]	6M
	b)	Explain the separating the DC Analysis and the Signal Analysis.	[L2] [CO4]	4M
3		For the below amplifier, let $V_{DD}=5V$, $R_D = 10K\Omega$, $V_t = 1V$, $K'_n = 20 \mu A/V^2$, $W/L = 20$, $V_{GS}=2V$, and $\lambda = 0$. Determine i) the dc current I_D and dc voltage V_{DS} ii) g_m iii) Voltage gain iv) If $V_{GS} = 0.2 \sin \omega t$, find V_{DS}	[L3] [CO3]	10M
				
4		Explain the operation of Small-Signal Equivalent-Circuit Models for: i) Neglecting the dependence of i_D on v_{DS} in saturation ii) Including the effect of channel length modulation, modulated	[L2] [CO3]	10M
5	a)	Define the MOSFET Transconductance g_m with mathematical expression.	[L1] [CO2]	6M
	b)	A MOSFET is to operate at $I_D = 0.1 \text{ mA}$ and is to have $g_m = 1 \text{ mA/V}$. If $K'_n = 2$	[L3] [CO3]	4M
6		Develop and Illustrate the T Equivalent-Circuit Model for the MOSFET.	[L3] [CO5]	10M
7	a)	Evaluate the overall voltage gain of the Common-Source Amplifier with a Source Resistance with suitable circuits.	[L5] [CO5]	6M
	b)	Build the equivalent circuit with the MOSFET represented by its T-Model.	[L3] [CO5]	4M
8	a)	Construct and Evaluate the overall voltage gain of the Common-Gate (CG) Amplifier with biasing circuit omitted.	[L5] [CO5]	6M
	b)	Develop the equivalent circuit of the CG amplifier with the MOSFET replaced with its T-Model.	[L6] [CO5]	4M
9	a)	Illustrate the need for Voltage Buffers or unity gain buffer amplifier with figures.	[L3] [CO5]	6M
	b)	List the important features of Source Follower.	[L1] [CO5]	4M

10	a)	A CS amplifier utilizes a MOSFET biased at $I_D = 0.25\text{Ma}$ with $V_{OV} = 0.25\text{V}$ and $R_D = 20\text{k}\Omega$. The device has $V_A = 50\text{V}$. The amplifier is fed with a source having $R_{sig} = 100\text{k}\Omega$, and a $20\text{k}\Omega$ load is connected to the output. Calculate R_{in} , A_{vo} , R_o , A_v and G_v .	[L4] [CO3]	6M
	b)	Compare the various parameters of CS, CG & CD amplifiers.	[L4] [CO6]	4M
11	a)	Derive the characteristic Parameters of the Source Follower with figures.	[L4] [CO4]	6M
	b)	Illustrate the MOSFET Transconductance g_m with graphical construction.	[L3] [CO2]	4M

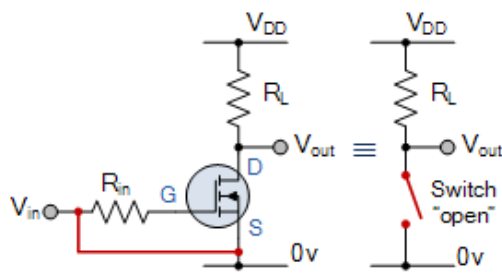Prepared by Dr. Nimmala Harathi, Ms. P. Alehya, Mr. C. C Manikanta
Department of ECE,
SIETK, Puttur.



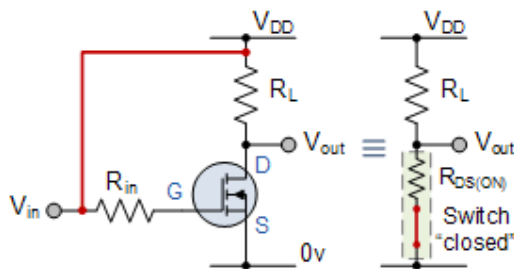- The input and Gate are grounded (0V)
- Gate-source voltage less than threshold voltage $V_{GS} < V_{TH}$
- MOSFET is "OFF" (Cut-off region)
- No Drain current flows ($I_D = 0$ Amps)
- $V_{OUT} = V_{DS} = V_{DD} = "1"$
- MOSFET operates as an "open switch"



- The input and Gate are connected to V_{DD}
- Gate-source voltage is much greater than threshold voltage $V_{GS} > V_{TH}$
- MOSFET is "ON" (saturation region)
- Max Drain current flows ($I_D = V_{DD} / R_L$)
- $V_{DS} = 0V$ (ideal saturation)
- Min channel resistance $R_{DS(on)} < 0.1\Omega$
- $V_{OUT} = V_{DS} \cong 0.2V$ due to $R_{DS(on)}$
- MOSFET operates as a low resistance "closed switch"