



**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

**Siddharth Nagar, Narayanavanam Road – 517583
QUESTION BANK (DESCRIPTIVE)**

Subject with Code: DIGITAL CIRCUITS DESIGN (23EC0403)

Course & Branch: B. Tech –ECE

Year & Semester: II - B. Tech. & I-Semester

Regulation: R23

UNIT- I

BOOLEAN ALGEBRA, LOGIC OPERATIONS, AND MINIMIZATION OF BOOLEAN FUNCTIONS

PART-A (2 MARKS)

1.	(a)	List out the types of number systems with one example for each.	[L2][CO1]	[2M]
	(b)	Convert $(41.6875)_{10}$ to Hexadecimal number.	[L5][CO1]	[2M]
	(c)	Write the truth table for $F=(A+B)(C+D)$	[L2][CO1]	[2M]
	(d)	What are Universal Gates? Give their truth tables.	[L1][CO1]	[2M]
	(e)	Perform the following Subtraction using 10's complement method. i) $3456 - 245$ ii) $631-745$	[L1][CO1]	[2M]

PART-B (10 MARKS)

2.	(a)	Convert the following numbers: i) $(AB)_{16}=()_2$ ii) $(1234)_8=()_{16}$ (iii) $(1000011)_2 = ()_{10}$	[L5][CO1]	[5M]
	(b)	Convert the following to binary and then to gray code. i) $(AB33)_{16}$ ii) $(BC54)_{16}$	[L5][CO1]	[5M]
3.		Convert the following: a) $(1AD)_{16}=()_{10}$ b) $(453)_8=()_{10}$ c) $(10110.0101)_2=()_{10}$ d) $(5436)_{10}=()_{16}$ e) $(647)_{10}=()_8$	[L6][CO1]	[10M]
4.	(a)	Perform the following subtraction by using 1's complement. i) $111001-1010$ ii) $0011-10001$	[L1][CO1]	[5M]
	(b)	Explain about the Binary Codes in detail.	[L1][CO1]	[5M]
5.	(a)	Prove De Morgan's theorems using Perfect Induction Method.	[L3][CO1]	[5M]
	(b)	Simplify the given boolean expression: $f = AB + \overline{AB}(\overline{AC})$	[L3][CO1]	[5M]
6.	(a)	Simplify the given Boolean expression to a sum of 3 terms. $A'C'D' + AC' + BCD + A'CD' + A'BC + AB'C'$	[L4][CO2]	[5M]
	(b)	Realize the following Boolean function using minimum number of logic gates. $f = \overline{x}yz + \overline{x}yz + \overline{x}y\overline{z} + \overline{x}yz$	[L4][CO2]	[5M]
7.		Obtain the Dual and complement to the following Boolean expressions. (i) $AB'C+AB'D+A'B'$ (ii) $A'B'C+ABC'+A'B'C'D$	[L1][CO2]	[10M]
8.		Illustrate the digital logic gates with graphical symbol, algebraic function and truth table.	[L2][CO1]	[10M]
9.		Express the following Boolean functions into Canonical form. i) $F1=AB+BC+CA$ ii) $F2= XY+Z+YZ+XYZ$	[L2][CO2]	[10M]

10.	(a)	Simplify the expression $f(x, y, z) = \sum (0, 1, 2, 3, 6, 7)$	[L4][CO3]	[5M]
	(b)	Obtain the simplified SOP and POS form of the following boolean expression, $Y = BC + AC' + AB + ABC$ using K-map.	[L1][CO3]	[5M]
11.	(a)	Simplify the Boolean expression, $F = A' + AB + ABD' + AB'D' + C'$ using Four Variable K-Map and draw the logic diagram using AOI logic.	[L4][CO3]	[5M]
	(b)	Simplify the expression in SOP form using don't cares. $Y = \sum (4, 5, 6, 8, 9) + d \sum (3, 7, 10, 11, 14, 15)$	[L4][CO3]	[5M]

UNIT- II
COMBINATIONAL LOGIC CIRCUITS
PART-A (2 MARKS)

1.	(a)	Define a Combinational Circuit and draw its block diagram.	[L1][CO4]	[2M]
	(b)	Define the following: i) Half adder and ii) Full Adder	[L1][CO4]	[2M]
	(c)	List the applications of encoder and decoder.	[L1][CO4]	[2M]
	(d)	What is a Priority encoder?	[L1][CO4]	[2M]
	(e)	Define Multiplexer and Demultiplexer.	[L1][CO4]	[2M]

PART-B (10 MARKS)

2.	(a)	Explain the procedure of designing a combinational logic circuit with an example.	[L2][CO4]	[5M]
	(b)	Design & implement Half Adder and Half subtractor logic circuits using AOI logic.	[L3][CO4]	[5M]
3.	(a)	Define a Full Adder and realize Full Adder circuit using two half adders.	[L3][CO4]	[5M]
	(b)	Design a Full Subtractor using truth table and realize Full subtractor circuit using two half subtractors.	[L3][CO4]	[5M]
4.	(a)	Design a 4 bit parallel adder/ Subtractor using full adders.	[L3][CO4]	[4M]
	(b)	Design & implement a 4-bit Binary-to-BCD code converter.	[L3][CO4]	[6M]
5.	(a)	Design & implement a 4-bit BCD -to-Excess-3 code converter.	[L3][CO4]	[5M]
	(b)	Construct a BCD Adder-circuit using 4-bit binary adders.	[L3][CO4]	[5M]
6.	(a)	Explain the working of a Carry- Look ahead adder with a neat logic diagram.	[L2][CO4]	[5M]
	(b)	Explain about Binary multiplier and realize its logic diagram.	[L2][CO4]	[5M]
7.	(a)	What is a Magnitude comparator? Design a 1-bit magnitude comparator and explain.	[L1][CO4]	[4M]
	(b)	Analyze the operation of a 2-bit magnitude comparator and derive the Boolean expressions for its outputs.	[L4][CO4]	[6M]
8.	(a)	What is encoder? Design an octal to binary encoder.	[L3][CO4]	[5M]
	(b)	Define Decoder and explain in detail about a 2 to 4 line binary decoder.	[L2][CO4]	[5M]
9.	(a)	Draw the circuit for 3 to 8 decoder and explain.	[L2][CO4]	[5M]
	(b)	Implement the full adder with decoder and two OR gates		
10.	(a)	Define Multiplexer. Construct 4:1 multiplexer with logic gates and truth table.	[L3][CO4]	[5M]
	(b)	Represent the following Boolean function with an 8:1 multiplexer. $F(A, B, C, D) = A'BD' + ACD + B'CD + A'C'D$.	[L2][CO4]	[5M]
11.	(a)	Implement the following Boolean function using 8:1 MUX $f(P, Q, R, S) = \sum (0, 1, 3, 4, 8, 9, 15)$	[L3][CO4]	[5M]
	(b)	What is Demultiplexer? Design an 1:8 demultiplexer using two 1:4 demultiplexers.	[L3][CO4]	[5M]



UNIT- III

HARDWARE DESCRIPTION LANGUAGE

PART-A (2 MARKS)

1.	(a)	Differentiate between Verilog and VHDL.	[L4][CO6]	[2M]
	(b)	Define the structural and behavioral representation of logic circuits.	[L1][CO6]	[2M]
	(c)	Explain about the module representation of logic circuits in Verilog.	[L1][CO6]	[2M]
	(d)	What are Verilog parallel case and full case statements?	[L2][CO6]	[2M]
	(e)	What is the Sensitivity list?	[L1][CO6]	[2M]

PART-B (10 MARKS)

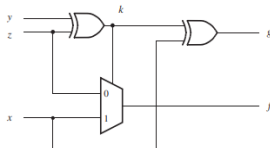 2.	a)	What is the syntax used to write a Verilog Code?	[L1][CO6]	[4M]
	b)	Write Verilog code to implement the following function: $f(x_1, x_2, x_3) = \sum m(0, 1, 3, 4, 5, 6)$ using the continuous assignment.	[L1][CO6]	[6M]
3.		Explain about the Hierarchical Verilog code with an example.	[L1][CO6]	[10M]
4.	a)	Write a Verilog code to implement the function, $f(x_1, x_2, x_3) = m(1, 2, 3, 4, 5, 6)$ using the gate-level primitives. Ensure that the resulting circuit is as simple as possible.	[L1][CO6]	[5M]
	b)	Write Verilog code that represents the logic circuit shown in Figure below. Use only continuous assignment statements to specify the required functions.	[L1][CO6]	[5M]
5.				
	a)	Write Verilog code for the following logic circuit diagram using behavioral structure representation.	[L1][CO6]	[5M]
6.				
	b)	Write an Verilog code for Half Adder and Full Subtractor with the help of Truth tables.	[L1][CO6]	[5M]
7.		Write Verilog code to implement the Boolean function $F = A' + AB + ABD' + AB'D' + C'$	[L1][CO6]	[10M]
7.	a)	Write an Verilog code for Full Adder with the help of Truth table.	[L1][CO6]	[5M]
	b)	Design an BCD adder and write the code for it in Verilog.	[L4][CO6]	[5M]
8.	a)	Explain Conditional operator in Verilog with an example.	[L2][CO6]	[5M]
	b)	Explain if-else statement in Verilog with an example.	[L2][CO6]	[5M]
9.	a)	State the importance of CAD Tools in HDL.	[L1][CO6]	[5M]
	b)	Explain case statement in Verilog with an example.	[L2][CO6]	[5M]
10.		Write an Verilog code for 2 Bit binary multiplier in structural Model.	[L1][CO6]	[10M]
11.	a)	Write an Verilog code for 16x1 MUX in behavioral Model.	[L1][CO6]	[5M]
	b)	State For loop statement in Verilog and explain the same with an example.	[L1][CO6]	[5M]

UNIT- IV
SEQUENTIAL LOGIC CIRCUITS

PART-A (2 MARKS)

1.	(a)	List the differences between Latch and Flip-flop.	[L4][CO4]	[2M]
	(b)	What is race around condition?	[L1][CO4]	[2M]
	(c)	Define a sequential circuit and draw its block diagram.	[L1][CO4]	[2M]
	(d)	List the applications of T flip flop.	[L1][CO4]	[2M]
	(e)	What is a Register?	[L1][CO4]	[2M]

PART-B (10 MARKS)

2.	a) Define a sequential logic circuit and sketch its block diagram.	[L1][CO4]	[3M]
	b) Differentiate between combinational and sequential circuits.	[L2][CO4]	[3M]
	c) Differentiate between synchronous and asynchronous sequential circuits.	[L2][CO4]	[4M]
3.	a) Define Latch and list different types of Latches.	[L1][CO4]	[3M]
	b) Define Flip-Flop. What are the different types of Flip-Flops?	[L1][CO4]	[3M]
	c) Explain the working principle of RS Flip-Flop with the help of logic diagram and give its Characteristic Table and Graphic symbol.	[L2][CO4]	[4M]
4.	a) With the help of logic diagram, obtain the characteristic table of D & T Flip-Flops. Also draw their graphic symbols.	[L2][CO4]	[5M]
	b) Explain the working principle of JK Flip-Flop in detail. Also give its characteristic equation, Graphic symbol and Excitation equation.	[L2][CO4]	[5M]
5.	a) Convert SR flip flop into JK Flip-Flop. Draw and explain its logic diagram.	[L2][CO4]	[5M]
	b) Design T Flip Flop using JK Flip-Flop and explain its logic diagram.	[L3][CO4]	[5M]
6.	a) Derive the excitation tables for SR, D, JK, and T Flip-Flops.	[L3][CO4]	[5M]
	b) Explain about the Ring counter in detail.	[L2][CO4]	[5M]
7.	a) Explain about the Johnson counter in detail.	[L2][CO4]	[5M]
	b) Define a counter and design a 4-bit Ripple counter.	[L1][CO4]	[5M]
8.	Design a 4 bit Decade counter.	[L4][CO4]	[10M]
9	What is a synchronous counter? Design a 3-bit synchronous up/down counter.	[L4][CO4]	[10M]
10.	Define a Shift register and explain its types.	[L2][CO4]	[10M]
11.	a) Write an Verilog code for 4- bit ring counter	[L1][CO6]	[5M]
	b) Design an 2-bit synchronous up-counter using Verilog Code.	[L6][CO6]	[5M]

UNIT- V
FINITE STATE MACHINES AND PROGRAMMABLE LOGIC DEVICES

PART-A (2 MARKS)

1.	(a)	What are the differences between Moore and Mealy Machines?	[L1][CO2]	[2M]
	(b)	List some of the limitations of finite state machines.	[L1][CO2]	[2M]
	(c)	State the types of ROM.	[L1][CO5]	[2M]
	(d)	List the major differences between PLA and PAL.	[L1][CO5]	[2M]
	(e)	List basic types of programmable logic devices.	[L1][CO5]	[2M]

PART-B (10 MARKS)

2.	a) Define Mealy model and explain it with neat diagram.	[L1][CO2]	[3M]
	b) Define Moore model. Explain it with neat diagram.	[L1][CO2]	[3M]
	c) Distinguish between Mealy & Moore machines.	[L2][CO2]	[4M]
3.	Explain the following related to sequential circuits with suitable examples: a) State diagram b) State table c) State assignment	[L2][CO2]	[10M]

4.	Derive the simplified sequential circuit for the following state table.	PS	Next State		Output	
			X=0	X=1	X=0	X=1
		A	a	b	0	0
		B	c	d	0	0
		C	a	d	0	0
		D	e	f	0	1
		E	a	f	0	1
		F	g	f	0	1
		G	a	f	0	1
5.	Determine the minimal state equivalent of the state table given.	PS	Next State		Output	
			X=0	X=1	X=0	X=1
		A	a	b	0	0
		B	c	g	0	1
		C	a	d	0	0
		D	e	f	0	1
		E	c	g	0	1
		F	a	b	0	0
		G	E	f	0	1
6.	Explain and Design a Sequence Detector.				[L2][CO5]	[10M]
7.	Explain in brief about Programmable Read Only Memory (PROM) with a suitable example.				[L2][CO5]	[10M]
8.	Illustrate the PLA for the following Boolean function. (i) $F_1 = \sum m(0,1,3,4)$ (ii) $F_2 = \sum m(1,2,3,4,5)$.				[L3][CO5]	[10M]
9.	Illustrate PLA for the following Boolean function. $F_1(A,B,C) = \sum m(3,5,7)$ $F_2(A,B,C) = \sum m(1,2,3,7)$				[L3][CO5]	[10M]
10.	Illustrate the PAL for the following Boolean functions. (i) $A(w,x,y,z) = \sum m(0,2,6,7,8,9,12,13)$ (ii) $B(w,x,y,z) = \sum m(0,2,6,7,8,9,12,13,14)$				[L3][CO5]	[10M]
11.	a) Draw and Briefly explain the basic structures of CPLD & FPGA				[L2][CO5]	[5M]
	b) Compare PROM,PLA & PLA				[L2][CO5]	[5M]