

**SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY:: PUTTUR
(AUTONOMOUS)**

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: Analog Circuits (23EC0459)

Course & Branch: B.Tech.–EEE

Regulation: R23

Year & Sem: II-B.Tech.& II-Sem.

UNIT –I

DIODE CLIPPING AND CLAMPING CIRCUITS

- | | | | | |
|-----|----|---|-----------|-------|
| 1. | a) | Define clipper and list types. | [L1][CO1] | [2M] |
| | b) | List the applications of clampers. | [L1][CO1] | [2M] |
| | c) | Discuss the need of biasing of a transistor. | [L2][CO1] | [2M] |
| | d) | Define operating point. | [L1][CO1] | [2M] |
| | e) | What is thermal Runaway? | [L1][CO1] | [2M] |
| 2. | a) | Explain positive and negative clippers with neat sketches | [L2][CO1] | [5M] |
| | b) | Explain about positive biased clippers with neat sketches | [L2][CO1] | [5M] |
| 3. | a) | Describe the operation of clipping at two independent levels | [L2][CO1] | [5M] |
| | b) | Draw the transfer characteristics of clippers and explain. | [L2][CO1] | [5M] |
| 4. | a) | Draw the circuit diagram of positive clamper and input & output wave forms. | [L2][CO1] | [5M] |
| | b) | Describe the operation of negative clamper circuit with neat diagram | [L2][CO1] | [5M] |
| 5. | | Describe the operation of Biased Positive Clipper circuit with neat diagram | [L2][CO1] | [10M] |
| 6. | a) | Comparison between clipping and clamping circuits. | [L2][CO1] | [4M] |
| | b) | List out the different types of clipping and clamping circuits. | [L1][CO1] | [6M] |
| 7. | a) | Explain the concept of DC and AC Load lines and discuss the Criteria for fixing the Q-point. | [L2][CO2] | [5M] |
| | b) | Draw the Fixed bias circuit and derive an expression for the stability factor. | [L2][CO2] | [5M] |
| | a) | Compare the various biasing techniques of a BJT. | [L2][CO2] | [4M] |
| 8. | b) | Draw the self-bias circuit and derive an expression for the stability factor. | [L4][CO2] | [6M] |
| 9. | | Consider the self-bias circuit where $V_{CC} = 22.5$ volts, $R_C = 5.6k\Omega$, $R_2 = 10k\Omega$ and $R_1 = 90k\Omega$, $h_{fe} = 55$, $V_{BE} = 0.6V$. the transistor operates in active region. Determine i) Operating point ii) stability factor. | [L3][CO6] | [10M] |
| 10. | a) | Draw the collector to base bias circuit and derive an expression for the stability factor. | [L4][CO3] | [6M] |
| | b) | Why self-bias is more stable compared with other biasing methods. | [L2][CO2] | [4M] |
| 11. | | Explain Thermistor & Sensistor compensation techniques with circuit diagram. | [L2][CO2] | [10M] |

UNIT –II

Small signals modeling of BJT and Feedback amplifier

1.
 - a) List out four hybrid parameters [L1][CO2] [2M]
 - b) Sketch the Equivalent circuit of a transistor using h-Parameters. [L1][CO2] [2M]
 - c) Express the negative feedback amplifier. [L1][CO2] [2M]
 - d) List the characteristics of negative feedback amplifiers. [L1][CO2] [2M]
 - e) Compare positive feedback and negative feedback. [L2][CO2] [2M]
2. Derive the equations for voltage gain, current gain, Input impedance, and output admittance for a BJT using h-Parameter model for BJT Transistor. [L4][CO3] [10M]
3.
 - a) A CE amplifier has the h-parameters given by $h_{ie} = 1000 \Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 50$ and $h_{oe} = 25 \mu \text{ mho}$. If both the load and source resistances are $1 \text{ K}\Omega$, determine the current gain & voltage gain. [L3][CO3] [5M]
 - b) Discuss the frequency response of CE amplifier with a neat diagram. [L2][CO2] [5M]
4. Derive the equations for voltage gain, current gain, Input impedance, and output Impedance for a BJT using Approximate model in CC configuration. [L4][CO3] [10M]
5. For a CB transistor amplifier driven by a voltage source of internal resistance $R_s = 1200 \Omega$, the load impedance is resistor $R_L = 1000 \Omega$. The h-parameters are $h_{ib} = 22 \Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$ and $h_{ob} = 0.5 \mu \text{ A/V}$. Compute the current gain A_i , Input impedance R_i , voltage gain A_v , output impedance Z_o , A_{IS} & A_{VS} using simplified model. [L3][CO3] [10M]
6. Explain the concept of Feedback amplifier with block diagram and general structure. [L2][CO2] [10M]
7.
 - a) Sketch the four types of feedback amplifier topologies. [L3][CO2] [5M]
 - b) An RC coupled amplifier has a mid-frequency gain of 200 and a frequency response from 100 Hz to 20 kHz. A negative feedback network with $\beta = 0.02$ is incorporated into the amplifier circuit. Determine the new system performance. [L3][CO3] [5M]
8.
 - a) Describe the effect of input resistance for Voltage shunt feedback amplifier. [L2][CO3] [5M]
 - b) Describe the effect of input resistance for current shunt feedback amplifier. [L2][CO2] [5M]
9.
 - a) A voltage series negative feedback amplifier has a voltage gain without feedback of $A = 500$, input resistance $R_i = 3 \text{ k}\Omega$, output resistance $R_o = 20 \text{ k}\Omega$ and feedback ratio $\beta = 0.01$. Calculate the voltage gain A_f , input resistance R_{if} and output resistance R_{of} of the amplifier with feedback. [L3][CO2] [5M]
 - b) Enumerate the general characteristics of negative feedback amplifiers [L1][CO2] [5M]
10.
 - a) Describe the effect of output resistance for current shunt feedback amplifier. [L2][CO2] [5M]
 - b) An amplifier has voltage gain with feedback of 100. If the gain without feedback changes by 20% and the gain with feedback should not vary more than 2%, determine the values of open loop gain A and feedback ratio β . [L2][CO3] [5M]
11.
 - a) Describe the effect of output resistance for Voltage series feedback amplifier. [L2][CO2] [5M]
 - b) Describe the effect of Input resistance for Voltage series feedback amplifier. [L2][CO2] [5M]

Unit III

Oscillator circuit

- | | | | | |
|-----|----|---|-----------|-------|
| 1. | a) | List out different types of oscillator? | [L1][CO1] | [2M] |
| | b) | What is the necessary condition for sustained oscillations? | [L1][CO1] | [2M] |
| | c) | Define op-amp. | [L1][CO1] | [2M] |
| | d) | What is slew rate? | [L1][CO1] | [2M] |
| | e) | Draw the IC 741 op-amp pin configuration. | [L1][CO1] | [2M] |
| 2. | a) | Explain Barkhausen criterion for oscillations with suitable diagram. | [L2][CO1] | [5M] |
| | b) | Interpret the various types of oscillators. | [L2][CO1] | [5M] |
| 3. | a) | Determine the condition for sustained oscillations for an RC phase shift Oscillator with necessary circuit diagrams. | [L3][CO3] | [5M] |
| | b) | Determine the frequency of oscillations when an RC phase shift oscillator has $R=10\text{ k}\Omega$, $C=0.01\mu\text{F}$ and $R_C = 2.2\text{ k}\Omega$. | [L3][CO6] | [5M] |
| 4. | a) | Explain the working principle of Wein-bridge oscillator using BJT and Derive the expression for frequency of sustained oscillations. | [L4][CO3] | [5M] |
| | b) | In a Wien bridge oscillator, if the value of R is $100\text{ k}\Omega$ and frequency of oscillation is 10kHz , examine the value of capacitor C. | [L3][CO6] | [5M] |
| 5. | a) | Draw the circuit diagram of Colpitts crystal oscillator using BJT and show the expression for frequency of oscillations. | [L3][CO3] | [5M] |
| | b) | Sketch the symbol ,Equivalent circuit and relation between reactance and frequency of piezoelectric crystal | [L2][CO3] | [5M] |
| 6. | | A crystal has the following parameters: $L = 0.5\text{ H}$, $C_s = 0.06\text{ pF}$, $C_p = 1\text{ pF}$, and $R = 5\text{ k}\Omega$. Find the series and parallel resonant frequencies and the Q-factor of the crystal. | [L3][CO3] | [10M] |
| 7. | a) | Draw the schematic symbol of an op-amp and list the different terminals with their features. | [L1][CO1] | [5M] |
| | b) | Draw the equivalent circuit diagram of Op-amp and list out the ideal characteristics of an operational amplifier. | [L1][CO1] | [5M] |
| 8. | a) | For a given op-amp, $\text{CMMR} = 10^5$ and differential gain $A_d = 10^5$. Determine the common mode gain A_{cm} of the op-amp. | [L2][CO5] | [5M] |
| | b) | Discuss the term common mode rejection ration (CMMR) in op-amp. | [L2][CO5] | [5M] |
| 9. | a) | Explain AC characteristics of op-amp. | [L2][CO5] | [6M] |
| | b) | What are the features of IC 741 Op-amp? | [L1][CO3] | [4M] |
| 10. | a) | Explain the term slew rate and illustrate the importance in op-amp circuits. | [L2][CO5] | [6M] |
| | b) | An op-amp has a slew rate of $2\text{V}/\mu\text{s}$. What is the maximum frequency of an output sinusoidal its peak value of 5V at which the distortion sets in due to the slew rate limitation? | [L1][CO6] | [4M] |
| 11. | a) | Explain about block diagram of typical Op-amp in detail. | [L2][CO3] | [5M] |
| | b) | Explain DC characteristics of op-amp. | [L2][CO3] | [5M] |

Unit IV

Op-Amp Applications

- | | | | |
|-----|--|-----------|-------|
| 1. | a) Define common mode Rejection Ratio. | [L1][CO1] | [2M] |
| | b) Draw equivalent circuit of an ideal Op-Amp | [L1][CO1] | [2M] |
| | c) List out the specifications of 741 IC. | [L1][CO1] | [2M] |
| | d) List the applications of Astable Multivibrator | [L1][CO1] | [2M] |
| | e) What are the types of Multivibrators? | [L1][CO1] | [2M] |
| 2. | a) Explain the operation of inverting summing amplifier. | [L2][CO5] | [5M] |
| | b) For the Non-inverting amplifier, $R_1=1k\Omega$ and $R_f = 10k\Omega$. Calculate the closed-loop voltage gain of the amplifier and the feedback factor β | [L3][CO6] | [5M] |
| 3. | a) Draw the circuit diagram of subtractor using Op-amp and explain its operation. | [L2][CO5] | [5M] |
| | b) Explain about Non Inverting AC amplifier using Op-amp? | [L2][CO4] | [5M] |
| 4. | a) For a V-I converter $V_{in} = 5V$, $R = 10k\Omega$, $V_1 = 1V$, Find the load current and output voltage V_o . Assume the Op-amp is initially nulled. | [L3][CO6] | [5M] |
| | b) Design a differentiator circuit with sine wave input using op-amp. | [L6][CO5] | [5M] |
| 5. | a) Discuss applications of I to V converters i) Photo detector ii) Photo FET detector. | [L2][CO5] | [5M] |
| | b) Design an op-amp differentiator that will differentiate an input signal with $f_{max} = 100$ Hz | [L6][CO6] | [5M] |
| 6. | a) List out the applications of analog multiplier and draw the schematic symbol of multiplier. | [L1][CO5] | [5M] |
| | b) Explain the operation of integrator using op-amp with a neat circuit diagram and draw the input-output waveforms. | [L2][CO5] | [5M] |
| 7. | Explain about Instrumentation amplifier with neat circuit diagram. | [L2][CO4] | [10M] |
| | Explain the operation of triangular wave generator using op-amp, with a neat circuit diagram and its waveforms. | [L2][CO4] | [10M] |
| 8. | | | |
| 9. | a) Explain about square wave generator with neat diagram using op-amp. | [L2][CO4] | [5M] |
| | b) Draw the circuit of Basic log amplifier and explain its operation. | [L2][CO5] | [5M] |
| 10. | a) Explain the operation of monostable multivibrator using op-amp, with a neat circuit and its waveforms | [L2][CO6] | [5M] |
| | b) List the different types of comparators and draw the transfer characteristics of ideal and practical comparator. | [L1][CO4] | [5M] |
| 11. | a) Draw the circuit diagram of Non-Inverting comparator & explain its operation. | [L2][CO4] | [5M] |
| | b) How does the sample and hold circuit operate during the "sample" mode. | [L2][CO4] | [5M] |

Unit V

Op-Amp Applications

1. a) Draw the pin configuration of 555 timer. [L1][CO1] [2M]
 b) What is a phase locked loop? [L1][CO1] [2M]
 c) List out the examples of digital phase detectors. [L1][CO1] [2M]
 d) Define monostable multivibrator. [L1][CO1] [2M]
 e) What are the specifications of ADC and DAC? [L1][CO1] [2M]
2. a) Explain about 555 timer functional diagram. [L2][CO1] [5M]
 b) Discuss about Schmitt trigger using 555 IC. [L2][CO1] [5M]
3. a) Draw a neat circuit of astable multivibrator using 555 IC and explain operation with waveforms. [L2][CO5] [5M]
 b) In the astable multivibrator, $R_A = 2.2k\Omega$, $R_B = 3.9k\Omega$ and $C = 0.1\mu F$. Determine the positive pulse width t_c , negative pulse width t_d and free-running frequency f_o . [L3][CO6] [5M]
4. a) Explain the operation of monostable multivibrator using 555 IC, with a neat circuit and its waveforms [L2][CO5] [5M]
 b) Draw SE566 VCO connection diagram and explain its operation. [L2][CO5] [5M]
5. Explain about PLL principle in detail and block diagram [L2][CO5] [10M]
6. a) Explain the Binary weighted resistor DAC with a neat diagram. [L2][CO4] [5M]
 b) Draw the circuit diagram of inverted R-2R DAC and explain its operation. [L2][CO4] [5M]
7. a) Explain in detail about R-2R DAC with a neat diagram. [L2][CO4] [5M]
 b) The basic step of a 9 bit DAC is 10.3 mV. If “000000000” represents 0 V. What output is produced if the input is “101101111”? [L3][CO6] [5M]
8. Consider a 4 bit R-2R ladder DAC of the a) Given $R = 10k\Omega$ and $V_R = 10V$. Determine the value of the feedback resistance R_f for the following output condition. [L2][CO6] [10M]
 - i) Value of 1 LSB at the output is 0.5V.
 - ii) Analog output is 6V for a binary input of 1000.
 - iii) Full scale output voltage is 10V.
9. Explain about the flash type ADC using op-amp with the truth table using 8 by 3 priority encoder. [L2][CO4] [10M]
10. Draw the circuit diagram of Dual Slope ADC and explain its working with neat sketches. [L2][CO4] [10M]
11. Discuss the parameters specifications of DAC/ADC. [L2][CO4] [10M]