



SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY :: PUTTUR

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)

Subject with Code: A&D IC Applications (23EC0412)

Course & Branch: B.Tech – ECE

Year & Sem: III-B.Tech & I-Sem

Regulation: R23

UNIT –I
ICS AND OP-AMPS

PART-A (2 MARKS)

1	a)	Define an Integrated Circuit.	[L1] [CO1]	2M
	b)	List classifications of ICs.	[L1] [CO1]	2M
	c)	State two characteristics of an ideal Op-Amp.	[L1] [CO1]	2M
	d)	What is the input impedance of an ideal Op-Amp?	[L1] [CO1]	2M
	e)	Define CMRR	[L1] [CO1]	2M

PART-B (10 MARKS)

2	a)	Write the advantages of Integrated Circuits.	[L1][CO1]	3M
	b)	Explain about the Levels of Integrations.	[L2][CO1]	7M
3	a)	Represent the symbol of IC 741 op-amp and Mention the 8 pins.	[L1][CO1]	3M
	b)	Draw the Symbol of an Op-Amp and Describe about the Op-Amp.	[L2][CO1]	7M
4	a)	Define Inverting Amplifier.	[L1][CO2]	3M
	b)	With the help of IC 741, illustrate the circuit of an inverting amplifier and explain its operation.	[L3][CO2]	7M
5	a)	Define Non-Inverting Amplifier.	[L1][CO1]	3M
	b)	Draw and Explain about the Non-Inverting Amplifier.	[L3][CO2]	7M
6	a)	Write about the Ideal Operational Amplifier.	[L1][CO1]	4M
	b)	Describe about the Differential gain and Common Mode gain.	[L2][CO1]	6M
7	a)	Explain about the Common Mode Rejection Ratio.	[L2][CO2]	4M
	b)	Show the Relationship between CMRR and Output Voltage of an Op-Amp.	[L3][CO2]	6M
8	a)	Illustrate the internal circuit of an operational amplifier	[L2][CO1]	3M
	b)	Illustrate the block diagram of an operational amplifier and discuss the role of its different stages.	[L2][CO1]	7M
9	a)	Write the DC Characteristics of an Op-Amp.	[L1][CO1]	7M
	b)	Write the AC Characteristics of an Op-Amp.	[L1][CO1]	3M
10	a)	Write the Features of an IC741 Op-Amp.	[L1][CO1]	3M
	b)	For an Op-Amp, CMRR & Differential mode gain is 10^5 .the output voltage changes by 20V in 4 micro sec.Calculate (i) Common Mode gain (ii) Slew rate	[L3][CO2]	7M
11	a)	Determine the output voltage of a differential Amplifier for the input voltages of $300\mu\text{V}$ & $240\mu\text{V}$.The Differential gain of the amplifier is 5000.the value of the CMRR is 100.	[L4][CO2]	5M
	b)	Determine the output voltage of a differential Amplifier for the input voltages of $400\mu\text{V}$ & $340\mu\text{V}$.The Differential gain of the amplifier is 5000.the value of the CMRR is 100.	[L4][CO2]	5M

UNIT –II
APPLICATIONS OF OP-AMP

PART-A (2 MARKS)

1	a)	What is an inverting amplifier?	[L1][CO2]	2M
	b)	Define a sample and hold circuit.	[L1][CO3]	2M
	c)	Define Virtual Ground Property.	[L1][CO2]	2M
	d)	Define comparator.	[L1][CO3]	2M
	e)	What is a Schmitt Trigger?	[L1][CO3]	2M

PART-B (10 MARKS)

2	a)	Explain the working of an inverting amplifier with Op-Amp and derive its voltage gain equation.	[L3][CO2]	5M
	b)	Express and Explain about the Non-Inverting Amplifier.	[L3][CO2]	5M
3	a)	Using an ideal op-amp, derive the expression for Vout of an inverting adder and describe how the circuit works.	[L3][CO2]	5M
	b)	Show the derivation for the non-inverting summing amplifier and explain the role of each component.	[L3][CO2]	5M
4	a)	Illustrate the inverting subtractor using an op-amp, derive the mathematical expression for Vout and explain its principle.	[L3][CO2]	5M
	b)	With the help of an op-amp, derive the working equation for a non-inverting subtractor circuit and discuss its principle.	[L3][CO2]	5M
5	a)	Explain the working of an instrumentation amplifier using its circuit diagram	[L2][CO2]	5M
	b)	Using the standard three-op-amp configuration, derive the gain formula of an instrumentation amplifier.	[L3][CO2]	5M
6	a)	With the help of a neat diagram, derive and explain the operation of an inverting AC amplifier.	[L3][CO2]	5M
	b)	Derive the mathematical expression for the voltage gain of a non-inverting AC amplifier and explain.	[L3][CO2]	5M
7	a)	Illustrate the circuit of an op-amp based V–I converter and describe how it converts an input voltage into a proportional current.	[L3][CO2]	5M
	b)	With a neat diagram, explain the working principle of an I–V converter and derive the output voltage expression.	[L3][CO2]	5M
8	a)	Obtain the expression for the transfer function of an inverting integrator circuit using an op-amp.	[L3][CO2]	5M
	b)	Illustrate the Expression of Differentiator Circuit.	[L3][CO2]	5M
9	a)	Describe the principle of a sample and hold circuit with the help of a neat circuit diagram.	[L2][CO3]	5M
	b)	How logarithmic and antilogarithmic amplifiers are implemented using op-amps? Draw and explain their circuits.	[L3][CO3]	5M
10	a)	Draw the schematic of an inverting comparator and explain its function with input-output waveforms.	[L3][CO3]	5M
	b)	Discuss about Schmitt trigger with neat circuit diagram and waveforms.	[L3][CO3]	5M
11	a)	Differentiate between Comparator and Schmitt Trigger.	[L2][CO3]	6M
	b)	Design an Adder Circuit using an Op-Amp to get the output voltage expression as $V_0 = -(0.1V_1 + V_2 + 10V_3)$	[L6][CO2]	4M

UNIT –III
ACTIVE FILTERS AND OTHER ICS
PART-A (2 MARKS)

1	a)	Define filter?	[L1][CO4]	2M
	b)	Define cut-off frequency.	[L1][CO4]	2M
	c)	List applications of 555 timer.	[L1][CO4]	2M
	d)	Define PLL?	[L1][CO4]	2M
	e)	Write the function of a phase detector.	[L1][CO4]	2M

PART-B (10 MARKS)

2	a)	Explain about the Low Pass Filter.	[L2][CO4]	4M
	b)	Design a 1 st Order Low Pass Butterworth Filter using an Op-Amp with Expressions.	[L3][CO4]	6M
3	a)	Explain about the High Pass Filter.	[L2][CO4]	4M
	b)	Design a 1 st Order High Pass Butterworth Filter using an Op-Amp with Expressions.	[L3][CO4]	6M
4	a)	Draw and Explain about the Band Pass Filter.	[L2][CO4]	5M
	b)	Draw and Explain about the Band Rejection Filter.	[L2][CO4]	5M
5	a)	Design a 2 nd Order Low Pass Butterworth Filter using an Op-Amp with Expressions.	[L3][CO4]	6M
	b)	Derive and Explain about the All Pass Filter.	[L3][CO4]	4M
6	a)	Discuss about the Pin Diagram of IC555 Timer.	[L2][CO4]	4M
	b)	Explain about the Functional description of IC555 Timer.	[L2][CO4]	6M
7	a)	Explain the working of a monostable multivibrator using IC 555 with a neat circuit diagram and waveforms.	[L2][CO4]	5M
	b)	Describe the operation of an astable multivibrator using IC 555 timer with the help of a circuit diagram.	[L2][CO4]	5M
8	a)	Illustrate the circuit of a Schmitt Trigger using IC 555 and explain its principle with transfer characteristics.	[L2][CO4]	5M
	b)	Draw and explain the block diagram of the monolithic IC 565 (PLL).	[L2][CO4]	5M
9	a)	With a neat block schematic, explain the functional operation of a Phase Locked Loop (PLL)	[L2][CO4]	6M
	b)	Define PLL and List the applications of PLL.	[L1][CO4]	4M
10	a)	Design a Low pass filter at a cutoff frequency of 10KHZ with a passband gain of 2.	[L3][CO4]	5M
	b)	Design a wideband pass filter having $f_L=400\text{HZ}$ $f_H=2\text{KHZ}$ pass band gain of 4. Draw the frequency response of the filter and calculate the Q Value of the filter.	[L4][CO4]	5M
11	a)	For the All pass filters, the values of R & C are $7.5\text{K}\Omega$ and $0.02\mu\text{F}$ respectively. if the input frequency is 1.5KHZ calculate the Phase shift.	[L3][CO4]	7M
	b)	Design a Notch filter to eliminate 120HZ hum.	[L6][CO4]	3M

UNIT –IV
VOLTAGE REGULATORS AND CONVERTERS
PART-A (2 MARKS)

1	a)	What is a voltage regulator?	[L1][CO5]	2M
	b)	Define ADC.	[L1] [CO5]	2M
	c)	Define DAC.	[L1] [CO5]	2M
	d)	Define Switching Regulator?	[L1] [CO5]	2M
	e)	Write the Types of ADC and DAC techniques.	[L1] [CO5]	2M

PART-B (10 MARKS)

2	a)	Draw and Explain about the Series Op-Amp Regulator.	[L3][CO5]	5M
	b)	Explain about the Voltage Regulators.	[L2][CO5]	5M
3	a)	Explain about the Switching Regulator.	[L2][CO5]	7M
	b)	Write the Applications of Voltage Regulators.	[L1][CO5]	3M
4	a)	Explain the basic structure of DAC.	[L2][CO5]	5M
	b)	Draw and explain the weighted resistor DAC.	[L3][CO5]	5M
5	a)	Draw and explain the operation of R-2R DAC.	[L3][CO5]	8M
	b)	List the types of ADC.	[L1][CO5]	2M
6	a)	Explain about parallel comparator ADC with neat block diagram.	[L2][CO5]	5M
	b)	Explain about counter type ADC with neat block diagram.	[L2][CO5]	5M
7	a)	The basic step of a 9-bit DAC is 10.3 mV. If “000000000” represents 0V. What output is produced if the input is “10110111”?	[L3][CO5]	3M
	b)	Explain about flash type ADC.	[L2][CO5]	7M
8	a)	Draw and explain successive approximation type ADC with an Example.	[L3][CO5]	5M
	b)	Draw the circuit diagram of Dual Slope ADC and explain its working with neat sketch.	[L3][CO5]	5M
9	a)	What output voltage would be produced by a D/A Converter whose output range is 0 to 10V & whose input binary no. is (i) 10 (2 bit DAC) (ii) 0110 (4 bit DAC) (iii) 10111100 (8 bit DAC)	[L3][CO5]	6M
	b)	Calculate the values of LSB and MSB and full scale output for an 8 bit DAC for the 0 to 10V range.	[L3][CO5]	4M
10	a)	An 8-bit DAC has an output voltage range of (0-2.55V) Define its Resolution in two ways.	[L3][CO5]	4M
	b)	The digital input for a 4-bit DAC is 0110. Calculate its final output voltage given $V_{OFS}=15V$.	[L3][CO5]	6M
11	a)	For a Dual slope ADC $V_R=100mV$ $t_1=50msec$ and clock frequency is 12KHZ find the digital output for an input voltage of 200mV.	[L4][CO5]	5M
	b)	An 8-bit has resolution of 20mV/LSB. find its V_{OFS} and V_O if the input is $(10000000)_2$	[L4][CO5]	5M



SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY :: PUTTUR

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (OBJECTIVE)

Subject with Code: A&D IC Applications (23EC0412)

Course & Branch: B.Tech – ECE

Year & Sem : III-B.Tech & I-Sem

Regulation: R23

UNIT –V
DIGITAL ICS

PART-A (2 MARKS)

1	a)	Define CMOS.	[L1][CO6]	2M
	b)	Define PMOS	[L1][CO6]	2M
	c)	Define NMOS	[L1][CO6]	2M
	d)	Define Encoder	[L1][CO6]	2M
	e)	Define Flipflop	[L1][CO6]	2M

PART-B (10 MARKS)

2	a)	Explain about the CMOS Logic Levels.	[L2][CO6]	5M
	b)	Draw and Explain about the PMOS Transistors.	[L3][CO6]	5M
3	a)	Draw and Explain about the NMOS Transistors.	[L3][CO6]	5M
	b)	Draw and Explain about the Basic CMOS Inverter.	[L3][CO6]	5M
4	a)	Design the NAND gate using CMOS Logic	[L3][CO6]	5M
	b)	Design the NOR gate Using CMOS Logic.	[L3][CO6]	5M
5	a)	Design and Explain about the CMOS AND-OR-INVERT	[L1][CO6]	5M
	b)	Design and Explain about the CMOS OR-AND-INVERT	[L1][CO6]	5M
6	a)	Write the Applications of TTL-74XX & CMOS 40XX Series ICs	[L2][CO6]	5M
	b)	Write the Specifications of TTL-74XX & CMOS 40XX Series ICs	[L2][CO6]	5M
7	a)	Define Decoder and Explain any one of the Decoder with truth table.	[L3][CO6]	5M
	b)	Define Encoder and Explain about any one of the Encoder with truth table	[L2][CO6]	5M
8	a)	Draw and Explain about the Priority Encoder.	[L2][CO6]	5M
	b)	Define Multiplexer and Explain any one of the Multiplexer with truth table.	[L1][CO6]	5M
9	a)	Define De-Multiplexer and Explain any one of the De-Multiplexer with truth table.	[L3][CO6]	5M
	b)	Define Flip-Flop and Write the types of Flip-Flops.	[L3][CO6]	5M
10	a)	Draw and Explain about the JK Flip-Flop.	[L2][CO6]	5M
	b)	Draw and Explain about the SR Flip-Flop.	[L2][CO6]	5M
11	a)	Explain about the Counters.	[L2][CO6]	5M
	b)	Explain about the Shift Registers,	[L2][CO6]	5M

UNIT –I
ICS AND OP-AMPS

1. What is an Integrated Circuit (IC) []
A) power cable B) A small chip with many electronic components C) A software tool D) A motor
2. What does IC classification depend on []
A) Color of the chip B) Voltage rating only C) Physical size D) No. of components & usage
3. What is the most used Op-Amp IC []
A) IC 555 B) IC 741 C) IC 7805 D) IC 4001
4. What is the function of an operational amplifier []
A) Convert AC to DC B) Generate power C) Store data D) Amplify electrical signals
5. What is the ideal input impedance of an Op-Amp []
A) 0 ohms B) 100 ohms C) 10 ohms D) Infinite
6. What is the ideal output impedance of an Op-Amp []
A) 1000 ohms B) 1 ohm C) Zero D) Infinite
7. What is the typical open-loop gain of an ideal Op-Amp []
A) 1 B) 10 C) Infinite D) 100
8. How many terminals does IC 741 have []
A) 6 B) 10 C) 4 D) 8
9. What is the purpose of the inverting input []
A) Reverses the phase B) Adds power of input signal C) Filters signals D) Multiplies signals
10. What is the power supply range of IC 741 []
A) $\pm 1V$ B) 0V to 5V C) $\pm 5V$ to $\pm 18V$ D) 50V to 100V
11. Which pin is used for offset null in IC 741 []
A) Pin 2 B) Pin 1 and Pin 5 C) Pin 3 D) Pin 4
12. What is circuit complexity in ICs []
A) No. of components B) Shape of circuit in the IC C) Color of IC D) Material used
13. What is the use of the output pin in Op-Amp []
A) Power the IC B) Adjust input C) Start oscillation D) Give the amplified signal
14. What is the role of feedback in Op-Amps []
A) Increases noise B) Decreases speed C) Controls gain and stability D) Heats the circuit
15. What is a differential input []
A) Difference between two input voltages B) Sum of two inputs C) Input with same voltage D) Input of power supply
16. What is CMRR in Op-Amps []
A) Gain at output B) Power used C) Ability to reject common signals D) Input current
17. Which of these is NOT a DC characteristic of Op-Amp []
A) Frequency response B) Input bias current C) Offset voltage D) Input offset current
18. Which one is an AC characteristic of Op-Amp []
A) Offset voltage B) Input impedance C) O/P impedance D) Slew rate
19. What does “slew rate” mean []
A) Input voltage B) Offset current C) Rate of change of output voltage D) Bias voltage
20. What is the use of an offset null []
A) Supply power B) Increase gain C) Start oscillation D) Remove unwanted output when input is zero

21. Which IC package is used for 741 Op-Amp []
 A) BGA B) QFP C) TO-92 D) DIP
 (Dual Inline Package)
22. What is the function of the non-inverting input []
 A) Reverse phase B) Keep same phase C) Ground the signal D) Act as output
 of input signal
23. Op-Amps are generally used with which feedback []
 A) No feedback B) Negative feedback C) Positive feedback D) Mixed feedback
24. What is the unit of gain in Op-Amps []
 A) Amps B) Volts C) Decibels (dB) D) Ohms
25. Which pin in IC 741 is for +Vcc supply []
 A) Pin 1 B) Pin 4 C) Pin 7 D) Pin 8
26. What does a high input impedance mean []
 A) Op-Amp takes very little current from input B) Takes more power C) Voltage becomes high D) Output is blocked
27. How is IC chip size generally measured []
 A) In kilograms B) In millimeters or micrometers C) In liters D) In volts
28. Which factor increases circuit complexity []
 A) Size of IC B) Shape of IC C) Number of transistors and resistors D) Color of IC
29. Which property is true for ideal Op-Amps []
 A) Low gain B) High output impedance C) Infinite input impedance D) Low bandwidth
30. What happens if both Op-Amp inputs are equal []
 A) Output is zero B) Output is max C) Output is noisy D) Output is negative
31. What is PSRR in Op-Amps []
 A) Output noise B) Phase shift C) Peak signal ratio D) Power Supply Rejection Ratio
32. Which component is not inside Op-Amp internal circuit []
 A) Transistors B) Resistors C) Capacitors D) Inductors
33. How many stages are in Op-Amp internal circuit []
 A)1 B)2 C)5 D)3
34. What does the gain of an Op-Amp depend on []
 A) Size of the chip B) Feedback and circuit design C) Color of IC D) Shape of package
35. What does output voltage swing mean []
 A) Oscillation time B) Pin number C) Circuit error D) Max. voltage Op-Amp can output
36. Why is IC 741 called general purpose Op-Amp []
 A) It is used in many common applications B) It is very costly C) It is programmable D) It has no feedback
37. Which pin in IC 741 is used for -Vcc []
 A) Pin 7 B) Pin 4 C) Pin 2 D) Pin 1
38. Which configuration gives highest gain []
 A) Unity gain B) Non-inverting C) Open-loop D) Inverting
39. Which signal does an Op-Amp amplify []
 A) Power signal B) Difference between two inputs C) Supply voltage D) Clock pulse
40. Why is IC packaging important []
 A) It protects the chip and allows connection B) It makes IC colorful C) It changes voltage D) It controls temperature

UNIT –II

APPLICATIONS OF OP-AMP

1. In an inverting amplifier, the input is applied to the----- terminal. []
A) Non-inverting B) Inverting C) Output D) Offset
2. In a non-inverting amplifier, the output is in---- phase with input. []
A) Opposite B) Lagging C) Same D) Shifted
3. A differential amplifier amplifies the---- between two signals. []
A) Sum B) Difference C) Product D) Average
4. An Op-Amp adder combines multiple---- signals. []
A) Digital B) AC C) Constant D) Input voltage
5. An Op-Amp subtractor gives the---- of two inputs. []
A) Sum B) Difference C) Average D) None
6. . Instrumentation amplifiers are known for high----- []
A) Power output B) Accuracy and gain C) Noise D) Temperature
7. An AC amplifier can block ----- signals. []
A) AC B) DC C) RF D) Modulated
8. A V to I converter converts voltage into []
A) Power B) Resistance C) Current D) Frequency
9. A current-to-voltage converter is used in----- devices. []
A) Digital clocks B) Photodiodes C) Motor controllers D) Transmitters
10. An Op-Amp integrator gives -----of input. []
A) Time integral B) Derivative C) Constant D) Pulse
11. . A log amplifier uses the -----behavior of diodes []
A) Linear B) Constant C) Logarithmic D) None
12. Differentiator gives the ----- of input. []
A) Integral B) Average C) Frequency D) Rate of change
13. Sample and hold circuits are used in ----- systems. []
A) Oscillators B) Motors C) ADC D) AM Radios
14. Antilog amplifiers perform ----- operations. []
A) Subtraction B) Exponential C) Frequency D) Noise removal
15. Op-Amp multipliers multiply two -----signals. []
A) Digital B) Output C) Clock D) Analog
16. Comparators compare two voltages and give a ----- output. []
A) Sine wave B) Triangular C) Binary D) Random
17. A Schmitt trigger provides -----switching. []
A) Slow B) Noise-free and stable C) Linear D) None
18. Astable multivibrator produces -----output. []
A) Stable DC B) Pulse once C) Constant voltage D) Continuous square wave
19. Monostable multivibrator gives-----output for one trigger. []
A) Continuous B) Single pulse C) Oscillating D) Inverted
20. Bistable multivibrator has ----- stable states. []
A) 1 B) 3 C) 2 D) 4
21. Triangle wave generator gives a ----- output shape. []
A) Square B) Linear ramp up and down C) Sawtooth D) Sinusoidal
22. Square wave generators give ----- output. []
A) Smooth B) Sine C) Modulated D) High and low levels
23. Wein Bridge oscillator uses Op-Amps to generate -----waves. []
A) Square B) Sine C) Triangular D) Sawtooth

24. Phase shift oscillators generate ----- waves with Op-Amps []
 A) DC B) Pulse C) Sine D) No
25. Which amplifier configuration gives phase inversion []
 A) Non-inverting B) Inverting C) Voltage follower D) None
26. Which amplifier has gain = 1 []
 A) Inverting B) Differential C) Subtractor D) Voltage follower (buffer)
27. Which Op-Amp circuit combines signals []
 A) Integrator B) Comparator C) adder D) Schmitt trigger
28. Which application removes a DC level from the input signal []
 A) Adder B) AC amplifier C) Subtractor D) Log amplifier
29. Which circuit is used to store input voltage briefly []
 A) Differentiator B) Integrator C) Sample and hold D) Comparator
30. What is the function of a comparator []
 A) Subtract voltages B) Add signals C) Multiply inputs D) Compare voltages and give digital O/P
31. What does a Schmitt trigger help eliminate []
 A) DC B) AC C) Gain D) Noise in signals
32. What is the output of a differentiator []
 A) Constant B) Rate of change C) Sine wave D) Amplified signal
33. What is the output of an integrator []
 A) Derivative B) Inverted input C) Cumulative sum over time D) No output
34. Op-Amp-based oscillators work without any ----- signal. []
 A) Voltage B) Gain C) Input D) Output
35. Triangular wave output is generated by combining which circuits []
 A) Differentiator only B) Comparator C) Subtractor D) Integrator and square wave generator
36. Which circuit is best for analog multiplication []
 A) Adder B) Multiplier using Op-Amp C) Differentiator D) Voltage follower
37. Which waveform is symmetrical and used in testing []
 A) Sine B) Square C) Sawtooth D) DC
38. Which application is important in ADCs using Op-Amps []
 A) Oscillator B) Sample and hold C) Schmitt trigger D) Adder
39. Which amplifier rejects common signals and amplifies difference []
 A) Non-inverting B) Adder C) Differential amplifier D) Comparator
40. Why is IC packaging important []
 A) Protects the chip & allows connection B) It makes IC colorful C) It changes voltage D) It controls temperature

UNIT –III

ACTIVE FILTERS AND OTHER ICS

1. Butterworth filters are designed for -----response. []
 A) Sharp B) Flat C) Uneven D) Rippled
2. A first-order low-pass filter allows ----- frequencies to pass []
 A) High B) Mid C) Low D) None
3. A second-order high-pass filter attenuates ----- frequencies more. []
 A) Low B) High C) All D) None
4. Band-pass filters allow a -----range of frequencies. []
 A) Very low B) Specific C) All D) None
5. A band-reject filter blocks ----- frequencies. []
 A) Low B) High C) Certain D) All
6. An all-pass filter passes all frequencies with ----- change. []
 A) Gain B) Phase C) Frequency D) Resistance
7. The cut-off frequency of a filter is the point where gain drops by ----- dB. []
 A) 0 B) 3 C) 6 D) 10
8. The IC 555 is commonly used as a----- []
 A) Comparator B) Filter C) Amplifier D) Timer
9. In the IC 555 timer, pin 3 is the ----- pin. []
 A) Trigger B) Reset C) Output D) Control
10. Pin 2 of IC 555 is the -----input. []
 A) Discharge B) Trigger C) Output D) Vcc
11. . In astable mode, IC 555 continuously produces a -----waveform. []
 A) Sine B) Square C) Triangular D) DC
12. In monostable mode, the IC 555 gives ----- output pulse(s) per trigger. []
 A) Continuous B) One C) Two D) Infinite
13. Which components decide the timing interval in a 555 timer []
 A) Transistors B) Inductors C) Diodes D) Resistors and capacitors
14. The IC 555 works with voltages from ----- volts. []
 A) 1–3V B) 3–6V C) 4.5–15V D) 20–25V
15. What is the function of the discharge pin in IC 555 []
 A) Output B) Discharges capacitor C) Inverts signal D) Controls voltage
16. A Schmitt trigger using Op-Amp introduces----- []
 A) Hysteresis B) Filtering C) Delay D) Gain
17. A Phase-Locked Loop (PLL) is used to lock onto the ----- of a signal. []
 A) Power B) Shape C) Frequency D) Voltage
18. The heart of a PLL is the----- []
 A) Filter B) Timer C) Comparator D) Phase detector & VCO
19. The IC 566 is a----- []
 A) Timer B) VCO C) Counter D) Amplifier
20. What is the use of the low-pass filter in a PLL []
 A) Increases voltage B) Stores data C) Acts as an amplifier D) Removes high-frequency components
21. The output frequency of a VCO depends on----- []
 A) Input voltage B) Input current C) Control voltage D) Clock signal
22. A monolithic PLL is a PLL built into a---- []
 A) Transistor B) Capacitor C) Single IC D) Transformer

- | | | | |
|-----|---|---|---|
| 23. | The function of a phase detector in PLL is to compare----- | [|] |
| | A) Voltages B) Input and feedback frequencies C) Currents D) Powers | | |
| 24. | A basic PLL has how many blocks | [|] |
| | A) 2 B) 4 C) 3 D) 5 | | |
| 25. | In filters, the roll-off rate of a second-order filter is ----- dB/decade. | [|] |
| | A) 10 B) 40 C) 20 D) 60 | | |
| 26. | The Butterworth filter provides -----in the passband. | [|] |
| | A) Peaks B) Flat response C) Ripple D) No gain | | |
| 27. | An astable 555 timer has no ----- state. | [|] |
| | A) Stable B) High C) Low D) Output | | |
| 28. | In monostable mode, output returns to low after----- | [|] |
| | A) Time period B) Triggering C) Reset D) Delay | | |
| 29. | The duty cycle of a 555 astable circuit depends on---- | [|] |
| | A) Load B) Vcc C) R1, R2, and C D) Pin 1 | | |
| 30. | A filter that passes high and low frequencies but blocks mid-range is called---- | [|] |
| | A) Low-pass B) Band-stop (Notch) C) Band-pass D) All-pass | | |
| 31. | What does a control voltage do in a VCO | [|] |
| | A) Sets amplitude B) Starts oscillator C) Changes output frequency D) Controls duty cycle | | |
| 32. | PLLs are commonly used in -----systems. | [|] |
| | A) Power supply B) Audio systems C) Communication D) Motors | | |
| 33. | The frequency of an IC 566 VCO is set by----- | [|] |
| | A) Inductance B) Resistor and capacitor C) Input power D) Output load | | |
| 34. | In a 555 timer, reset pin (pin 4) is used to----- | [|] |
| | A) Disable the timer B) Set frequency C) Start VCO D) Connect to Vcc | | |
| 35. | A band-pass filter is formed by combining----- | [|] |
| | A) Two low-pass filters B) Low-pass and high-pass filters C) High-pass filters only D) Schmitt triggers | | |
| 36. | The unit for phase in a PLL is----- | [|] |
| | A) Hz B) Degrees or radians C) Amps D) Volts | | |
| 37. | Which IC is used for generating accurate timing pulses | [|] |
| | A) 723 B) 741 C) 555 D) 4017 | | |
| 38. | The VCO in a PLL controls the ----- of output signal. | [|] |
| | A) Power B) Amplitude C) Frequency D) Duty | | |
| 39. | Filters are classified by their ----- characteristics. | [|] |
| | A) Frequency B) Voltage C) Current D) Size | | |
| 40. | The main use of filters in electronics is to----- | [|] |
| | A) Reduce size B) Change voltage C) Store energy D) Pass or block specific frequencies | | |

UNIT –IV

VOLTAGE REGULARS AND CONVERTERS

1. What does a voltage regulator do []
 A) Increases current B) Keeps output voltage constant C) Controls resistance D) Amplifies signal
2. A series Op-Amp regulator uses a ----- element in series. []
 A) Capacitor B) Resistor C) Pass transistor D) LED
3. IC 723 is a -----voltage regulator. []
 A) Fixed B) General purpose C) Switching D) AC
4. Which IC provides positive fixed voltage []
 A) 7912 B) 723 C) 555 D) 7812
5. What is the output of a 7805 regulator []
 A) 3.3V B) 5V C) 9V D) 12V
6. Switching regulators use -----to control voltage []
 A) Resistors B) Diodes only C) High-speed switching elements D) Capacitors only
7. A buck converter ----- the voltage. []
 A) Increases B) Decreases C) Inverts D) Blocks
8. A boost converter ----- the voltage. []
 A) Reduces B) Maintains C) Increases D) Discharges
9. In a switching regulator, efficiency is usually above ----- []
 A) 30% B) 50% C) 100% D) 70–90%
10. A DAC converts----- []
 A) A/D B) D/A C) AC to DC D) Voltage to current
11. In a weighted resistor DAC, each bit has a ----- resistor. []
 A) Same B) Infinite C) Zero D) Different weighted
12. R-2R Ladder DAC uses only ----- values of resistors. []
 A) Variable B) Three C) None D) Two
13. In an inverted R-2R DAC, output polarity is----- []
 A) Positive B) Alternating C) Floating D) Negative
14. What is the purpose of an ADC []
 A) Store signals B) Convert A/D C) Amplify current D) Reduce voltage
15. Flash ADC is also called ----- type. []
 A) SAR B) Dual slope C) Counter D) Parallel comparator
16. A counter-type ADC uses a ----- counter. []
 A) Decrementing B) Binary C) Analog D) Loop
17. Successive Approximation ADC uses a----- []
 A) Timer B) Ramp generator C) Binary search method D) Frequency counter
18. A dual-slope ADC is ----- but very accurate. []
 A) Fast B) Slow C) Inaccurate D) Unstable
19. Resolution of a DAC refers to----- []
 A) Power rating B) Smallest output change C) Clock speed D) Voltage input
20. Linearity of a DAC means []
 A) Output is random B) Follows sine wave C) Output changes uniformly D) No signal
21. Which component in a series regulator controls the output voltage []
 A) Zener diode B) Pass transistor C) Resistor D) Capacitor
22. A switching regulator improves efficiency by----- []
 A) Heating up B) Rapidly turning on and off C) Reducing frequency D) Increasing resistance

23. The IC 723 can be used for both ----- voltage regulation. []
 A) AC and DC B) Positive and negative C) High and low D) Steady and variable
24. Which type of regulator uses a reference voltage and comparator []
 A) Linear B) Thermoelectric C) Diode-only D) Switching
25. The dropout voltage in a linear regulator is the difference between----- []
 A) Load and input B) Ground and output C) Input and output D) Vcc and ground
26. Which regulator can be used to step up voltage []
 A) Buck B) Linear C) Boost D) Series
27. What is the main function of a buck-boost converter []
 A) Lower output only B) Raise output only C) Block DC D) Either increase or decrease output voltage
28. Which part of a switching regulator stores energy []
 A) Capacitor B) Inductor C) Transistor D) Zener diode
29. The IC 723 uses an internal reference voltage of about []
 A) 1.2V B) 3.3V C) 7.15V D) 9V
30. A DAC converts digital data to a/an ----- signal. []
 A) Binary B) Clock C) Analog D) Pulse
31. Which DAC type uses binary-weighted resistors []
 A) Weighted resistor B) R-2R DAC C) Flash DAC D) PWM DAC
32. What is the main advantage of an R-2R ladder DAC []
 A) Variable resistors B) Uses only two resistor values C) Needs high power D) No linearity
33. The resolution of an n-bit DAC is equal to---- []
 A) 1/n B) 1/(2ⁿ) C) 2ⁿ D) n²
34. What defines the speed of an ADC []
 A) Power rating B) Resolution C) Conversion time D) Clock voltage
35. Which ADC type is the fastest []
 A) Dual slope B) SAR C) Counter D) Flash
36. A successive approximation ADC has ----- speed and accuracy. []
 A) Low, low B) Medium, good C) High, low D) Low, high
37. Dual slope ADCs are used for ----- measurements. []
 A) High-speed B) AC C) Precision D) Wireless
38. In a dual slope ADC, the reference voltage is applied during the ----- phase. []
 A) Integration B) De-integration C) Sampling D) Delay
39. Monotonicity in DACs means output always ----- with input. []
 A) Stays same B) Decreases C) Resets D) Increases or stays constant
40. Linearity error in a DAC is the difference between actual and ----- output []
 A) Voltage B) Ideal C) Digital D) Clocked

UNIT –V

DIGITAL ICS

- | | | |
|-----|---|-------|
| 1. | CMOS logic gates consume ----- power.
A) High B) Low C) Medium D) No | [] |
| 2. | CMOS stands for -----.
A) Control Mode Operation B) Coded MOS Metal Oxide Semiconductor C) Complementary Metal Oxide Semiconductor D) Central MOS | [] |
| 3. | A basic CMOS inverter uses ----- transistors.
A) One B) Three C) Four D) Two (PMOS + NMOS) | [] |
| 4. | NAND and NOR are called ----- gates.
A) Secondary B) Universal C) Logicless D) Passive | [] |
| 5. | CMOS 4011 is a ----- gate IC.
A) NAND B) NOR C) AND D) OR | [] |
| 6. | TTL logic families start with number -----.
A) 4000 B) 74XX C) 555 D) 723 | [] |
| 7. | Code converters are used to convert ----.
A) Analog to Digital B) Clock to pulse C) Binary to BCD or Gray code D) None | [] |
| 8. | A decoder does the function of ---- input.
A) Multiplying B) Storing C) Inverting D) Activating one output based on binary input | [] |
| 9. | An encoder converts multiple inputs into a ---- code.
A) Sound B) Binary C) Pulse D) Digital | [] |
| 10. | A priority encoder gives output based on ----.
A) Sum B) Highest input priority C) Lowest signal D) Last input | [] |
| 11. | A multiplexer selects ---- input(s) for output.
A) Multiple B) Random C)) One D) All | [] |
| 12. | A demultiplexer routes input to ---- output(s).
A) One B)) Multiple C) Zero D) Single | [] |
| 13. | 7483 IC is used as ----.
A) 4-bit Binary Adder B) Decoder C) Flip-flop D) Comparator | [] |
| 14. | A magnitude comparator compares ----.
A) Voltages B) Binary numbers C) Clocks D) Frequencies | [] |
| 15. | Flip-Flops are ---- devices.
A) Combinational B) Analog C) Sequential D) Digital only | [] |
| 16. | A D Flip-Flop stores ---- bit.
A)2 B)1 C)4 D)8 | [] |
| 17. | A JK Flip-Flop has how many stable states?
A)3 B)4 C)2 D) None | [] |
| 18. | T Flip-Flop toggles when ----.
A) Input is low B) Input is high and clock pulses C) No clock D) Reset is active | [] |
| 19. | A synchronous counter changes state with ----.
A) Random input B) Input voltage C) Clock signal D) Noise | [] |
| 20. | A decade counter counts up to ----.
A)8 B)11 C)16 D)10 | [] |

21. Shift registers move data ----. []
A) Randomly B) In parallel C) Bit by bit D) In analog
22. 74LS194 is a ---- shift register. []
A) 4-bit bidirectional B) 8-bit C) 4-bit bidirectional D) Decoder
23. A ring counter is a type of ---- counter. []
A) Up-down B) Shift register-based C) Ripple D) Random
24. Shift registers can be used to convert ---- to ---- data. []
A) Serial to parallel B) Analog to digital C) Clock to signal D) Data to clock
25. 74LS194 is a ---- shift register IC. []
A) 8-bit B) 4-bit bidirectional C) 2-bit unidirectional D) Tri-state
26. A flip-flop is a basic storage element in ---- logic []
A) Linear B) Analog C) Sequential D) Parallel
27. Which gate is used in SR flip-flop design []
A) XOR B) NOR or NAND C) NOT D) OR
28. The master-slave JK flip-flop avoids ---- problems. []
A) Overvoltage B) Race-around C) Underclock D) Parity
29. Which flip-flop is used in most counters? []
A) D B) SR C) T D) Gated
30. Sequential circuits depend on ---- inputs. []
A) Voltage B) Resistor values C) Parallel buses D) Present input and past states
31. A ripple counter is also known as a ---- counter. []
A) Synchronous B) Ring C) Asynchronous D) Bidirectional
32. In ripple counters, flip-flops are triggered by the ---- output. []
A) Same B) Previous stage C) Clock directly D) Power supply
33. Which counter can count both up and down? []
A) Ring counter B) Ripple counter C) Up-down counter D) Johnson counter
34. The propagation delay in asynchronous counters is ----. []
A) Zero B) Accumulated per flip-flop C) Constant D) Negative
35. A Johnson counter is a type of ---- counter. []
A) Binary B) Ripple C) Shift register-based D) Full-adder
36. How many states does a 4-bit Johnson counter have? []
A) 4 B) 8 C) 16 D) $2n = 8$
37. What is the function of a clock in sequential circuits? []
A) Control voltage B) Supply power C) Synchronize data movement D) Add delay
38. . In a 4-bit synchronous counter, all flip-flops are triggered by the ----. []
A) Previous output B) Same clock C) Output of first FF D) Ground
39. Which IC is a 4-bit synchronous binary counter? []
A) 7400 B) 74151 C) 74161 D) 7474
40. Flip-flops are also called ---- devices. []
A) Timing B) Bistable C) Single-shot D) Cascade

Prepared by:

1. Mr. U.SRINIVASULU

Assistant Professor/ ECE

2. Mr. SV.RAJESH KUMAR

Assistant Professor / ECE