



SIDDHARTH INSTITUTE OF ENGINEERING & TECHNOLOGY: PUTTUR-517 583_
(AUTONOMOUS)

Siddharth Nagar, Narayanavanam Road – 517583

QUESTION BANK (DESCRIPTIVE)


Subject with Code : Power Electronic Converters (20EE2112) **Course & Branch:** M.Tech - PE

Year & Sem: I-M.Tech & II-Sem

UNIT-I

THYRISTOR

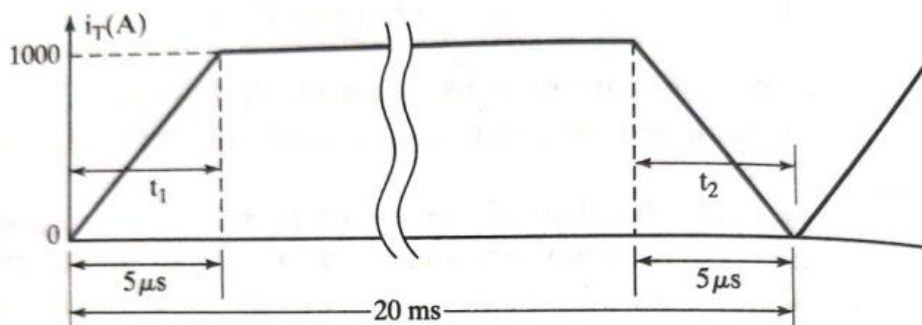1. Explain briefly about Silicon controlled Rectifiers. **L1,CO1[12M]**
2. What are the turn-off and turn-on characteristics of SCR? **L1, CO1[12M]**
3. What are the output and transfer characteristics of IGBTs **L1, CO1[12M]**
4. a) What is a bipolar transistor and what is the difference between SCR and BJT? **L1, CO1[6M]**
- b) Explain about steady state characteristics of BJT with neat sketch. **L1, CO1[6M]**
5. a) What is the purpose of shunt snubber and series snubber in transistor? **L1, CO1[6M]**
- b) A thyristor carries a current as shown in the figure and the current pulse is repeated at a frequency of $f_s=50\text{hz}$. Determine the average on-state current I_T . **L3, CO1[6M]**



6. a) What are the turn-off and turn-on characteristics of MOSFET? **L1, CO1[6M]**
- b) What is the switching model of n-channel MOSFET? **L1, CO1[6M]**
7. What is meant by commutation? Draw the line commutation and forced commutation circuit for Thyristors. **L3,CO1[12M]**
8. a) Draw and explain the turn-off and turn-on characteristics of MOSFET? **L3,CO1[6M]**

- b) Two MOSFETs that are connected in parallel ,carry a total current of $I_T=20A$.The drain to source voltage of MOSFET M_1 is $V_{DS1}=2.5V$ and that of MOSFET M_2 is $V_{DS2}=3V$.Determine the drain current of each transistor and difference in current sharing if the current sharing series resistances are a) $R_{S1}=0.3 \text{ ohm}$ and $R_{S2}=0.2 \text{ ohm}$,and b) $R_{S1}=R_{S2}=0.5\text{ohm}$. **L3,CO1[6M]**
9. Draw and Explain the dynamic characteristics of SCR? **L3,CO1[12M]**
10. a) Derive an expression for two transistor analogy of a thyristor and explain briefly. **L1,CO1,[12M]**
- b) Explain the construction of IGBT with neat diagram. **L3,CO1,[12M]**

R20

Course Code: 20EE2112

UNIT –II

SINGLE-PHASE &THREE-PHASE AC TO DC CONVERTER

1. Explain about single phase full converter with RL load. **L1, CO2 [12M]**
2. Explain about three-phase dual converter. **L1, CO2[12M]**
3. a) What is the pulse-width-modulation control of converters? **L1, CO2[6M]**
- b) The single phase full converter has a RL load having $L=6.5\text{mh}$, $R=0.5 \text{ ohm}$,and $E=10V$.the input voltage $V_s=120V$ at (rms) 60hz.Determine a)the load current I_{L0} at $wt= \alpha=60^0$ b)the average thyristor current, c)the rms thyristor current d) rms output current e) the critical delay angle **L2, CO2[6M]**
4. Explain the principle of operation of phase-controlled converter. **L1, CO2[12M]**
5. Explain the principle of operation of three-phase half-wave converters. **L1, CO2[12M]**
6. How does a 12 pulse converter works? and draw the circuit
7. State and explain different methods of control of converters. **L1, CO2[12M]**
8. Derive an output voltage equation for a three phase semi converter with neat circuit and waveforms. **L3, CO2 [12M]**
9. a) The single phase dual converter is operated from a 120v,60hz supply and load resistance is $R=10 \text{ ohm}$.The circulating inductance is $L_r=40 \text{ mH}$,delay angles are $\alpha_1=60^0$ and $\alpha_2=120^0$.calculate the peak circulating current and the peak current of converter 1. **L3, CO2,[6M]**
- b) What are the extinction angle controls of converters? **L1, CO2[6M]**
10. a) Derive an expression for average output current for single phase full converter with RL-Load. **L3, CO2[6M]**
- b) What are the reactive power considerations of ac-dc converters? **L1, CO2[6M]**

UNIT –III
DC-DC CONVERTERS

1. Explain the principle of step-down converter with RL-load. **L1 CO3[12M]**
2. Explain the principle and operation of the step-up converter with RL-load. **L1 CO4[6M]**
3. Classify the converters based on quadrant operation and explain in detail with neat diagrams. **L3 CO3[12M]**
4. Analyse the output voltage equation for operation of the step-up converter with neat circuit diagram. **L3 CO3[12M]**
5.
 - a) What is a dc-dc converter? **L1 CO3[6M]**
 - b) Derive an output voltage equation for a step down converter. **L3 CO3[6M]**
6. Explain the principle and operation of Buck converter. **L3 CO4[12M]**
7. With neat circuit diagram and waveforms explain the principle and operation of the Boost converter. **L2 CO4[12M]**
8. Draw the waveforms for operation of the Buck-Boost converter and explain. **L1 CO4[12M]**
9. With neat circuit diagram and waveform explain the principle and operation of the cuk converter. **L1 CO4[12M]**
10. Explain three phase controlled converters with neat sketch. **L1 CO4[12M]**

UNIT –IV
SINGLE-PHASE INVERTERS

1. Explain the principle of the Three-Phase bridge Inverter with neat circuit diagram and waveforms **L1 CO5 [12M]**
2. a) Classify the inverters based on different aspects. **L3 CO5 [6M]**
b) What is the difference between half-bridge and full-bridge inverters? **L1 CO5 [6M]**
3. Explain the principle and operation of the Voltage source inverters. **L1 CO5 [12M]**
4. Draw the waveforms for three-phase current source inverter and explain in detail. **L2 CO5 [12M]**
5. Explain the principle and operation of the current source inverters. **L1 CO5 [12M]**
6. Draw the waveforms for three-phase inverter when each transistor conducts for 120° . **L2 CO5 [12M]**
7. What are the techniques used for harmonic reductions in inverters? **L3 CO5 [12M]**
8. Evaluate the voltage control of Three-Phase inverters? **L3 CO5 [12M]**
9. Explain briefly about difference between space vector modulation and PWM technique. **L1 CO5 [12M]**
10. Compare the different types of modulation techniques used in inverters. **L3 CO5 [12M]**

UNIT –V
THREE PHASE INVERTERS

- | | | | |
|-----|--|---------|-------|
| 1. | Explain the principle of the Three-Phase Inverter. | L1, CO5 | [12M] |
| 2. | a) What are the types of inverters? explain in detail. | L1, CO5 | [6M] |
| | b) What is the difference between single-Phase and Three-Phase inverters? | L1, CO5 | [6M] |
| 3. | With neat circuit diagram explain the principle and operation of the series inverters. | L3, CO5 | [12M] |
| 4. | Explain the operation of single-phase inverter and draw the waveforms? | L3, CO6 | [12M] |
| 5. | What is parallel inverter ? and explain the operation with neat waveforms. | L1, CO6 | [12M] |
| 6. | Draw the waveforms for three-phase inverter when each transistor conducts for 180°. | L2, CO6 | [12M] |
| 7. | What are the voltage control techniques of three-phase inverters? | L1, CO5 | [12M] |
| 8. | Draw the waveforms for three-phase inverter when each thyristor conducts for 120°. | L3, CO6 | [12M] |
| 9. | Explain briefly about difference between voltage control and PWM technique. | L1, CO6 | [12M] |
| 10. | Explain the Pulse width modulation techniques used in inverters | L1, CO6 | [12M] |

PREPARED BY: Dr. M. PRIYA